

مفوضه ب (1):  
 $I_{max} = 10^4 \times 10^{-4} = 1 \text{ A}$  (الجواب B)

(2)  
 $E = \frac{1}{2} C U_{max}^2 = \frac{1}{2} \times 2 \times 10^{-5} \times (6)^2$

$E = 36 \times 10^{-5} \text{ J}$  (الجواب A)

(3)  
 $\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \omega'_0 = \frac{1}{\sqrt{L \times 2C}}$

(الجواب C)  
 $\omega'_0 = \frac{1}{\sqrt{2} \sqrt{LC}} = \frac{\omega_0}{\sqrt{2}}$

(4)  
 $T_0 = \frac{\lambda}{v} = 2\pi \sqrt{LC}$

$\frac{\lambda}{3 \times 10^8} = 2\pi \sqrt{10^{-3} \times 10^{-12}}$

$\lambda = 3 \times 10^8 \times 2 \sqrt{\pi^2 \times 10^{-15}}$

$\lambda = 6 \times 10^8 \sqrt{10^{-14}} = 6 \times 10^8 \times 10^{-7} = 60 \text{ m}$

(الجواب B)

(5)  
 $T_0 = 2\pi \sqrt{LC}$

$0.02 = 2\pi \sqrt{2\pi \times 10^{-3} C}$  نربح الطرفين

$4 \times 10^{-4} = 40 \times 2\pi \times 10^{-3} C \Rightarrow$

$C = \frac{4 \times 10^{-4}}{40 \times 2\pi \times 10^{-3}} = \frac{10^{-4}}{2\pi \times 10^2} = \frac{1}{200\pi}$

$C = \frac{1}{200\pi} \text{ F}$  (الجواب D)

(6)  
 $E = \frac{1}{2} C U_{max}^2 = \frac{1}{2} \times 20 \times 10^{-6} \times (500)^2$

$E = 10^{-5} \times 25 \times 10^4 = 2.5 \text{ J}$

هذا البنك المؤتمت لبحث الدارة المهتزة  
 قسم الطالب المنتهت

C (3) D (2) D (1)

C (6) A (5) B (4)

C (9) B (8) B (7)

D (12) C (11) B (10)

D (14) A (13)

قسم الطالب المنتهت

A (3) C (2) C (1)

A (6) D (5) C (4)

B (9) C (8) B (7)

D (12) A (11) B (10)

C (15) A (14) D (13)

A (18) D (17) A (16)

C (21) B (20) A (19)

A (24) B (23) D (22)

B (25)

قسم الطالب المنتهت

$I_{max} = \omega_0 q_{max} \dots (1)$

$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-2} \times 10^{-6}}} = \frac{1}{\sqrt{10^{-8}}} = 10^4 \text{ rad/s}$

$q_{max} = C \times U_{max} = 1 \times 10^{-6} \times 100 = 10^{-4} \text{ C}$

المدرس فراس قلعه جي  
 مبرور في التقاضيل التربوي  
 098440574

قسم لطالب بالمنقوش

$$f_0 = \frac{1}{T_0} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{10^{-3} \times 10^{-9}}} \quad (1)$$

$$f_0 = \frac{1}{2\pi\sqrt{10^{-12}}} = \frac{1}{2\pi \times 10^{-6}} = \frac{1}{2\pi} \times 10^6$$

$$f_0 = \frac{100 \times 10^4}{2\pi} = \frac{32\pi \times 10^4}{2\pi} = 16 \times 10^4 \text{ Hz}$$

الجواب (B)

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$f_0' = \frac{1}{2\pi\sqrt{\frac{L}{8} \times 2C}} = \frac{1}{2\pi\sqrt{\frac{1}{4}LC}}$$

$$f_0' = \frac{2}{2\pi\sqrt{LC}} = 2f_0$$

يزداد ذلك مثليين، الجواب (B)

$$f_0 = \frac{1}{T_0} = \frac{1}{2\pi\sqrt{LC}} \quad (11)$$

$$C = \frac{q}{U} = \frac{0.4 \times 10^{-6}}{200} = 2 \times 10^{-9} \text{ F}$$

$$L = 4\pi \times 10^{-7} \frac{N^2}{l} \text{ s}$$

$$N = \frac{l'}{2\pi r}, \quad S = \pi r^2 \quad (12)$$

$$\Rightarrow L = 4\pi \times 10^{-7} \frac{\frac{l'^2}{4\pi^2 r^2} \pi r^2}{\frac{l'}{2\pi r}} \Rightarrow$$

$$L = \frac{10^{-7} \times l'^2}{l} = \frac{10^{-7} \times 1600}{20 \times 10^{-2}}$$

$$L = 8 \times 10^{-4} \text{ H} \quad \text{نقوضه، (A)}$$

$$f_0 = \frac{1}{2\pi\sqrt{8 \times 10^{-4} \times 2 \times 10^{-9}}} = \frac{1}{8\pi\sqrt{10^{-13}}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 10^{-6} \times 10^{-8}}} = 10^7 \text{ rad}\cdot\text{s}^{-1} \quad (9)$$

الجواب (B)

$$U_{\text{max}} = \frac{q_{\text{max}}}{C} = \frac{10^{-4}}{10^{-6}} = 100 \text{ V} \quad (10)$$

الجواب (B)

$$I_{\text{max}} = \omega_0 q_{\text{max}} = 10^7 \times 10^{-6} = 0.1 \text{ A} \quad \text{الجواب (D)}$$

$$L = \frac{10^{-7} \times l'^2}{l} \Rightarrow 10^{-3} = \frac{10^{-7} \times l'^2}{100 \times 10^2} \quad (10)$$

$$\Rightarrow l'^2 = \frac{10^{-3} \times 100 \times 10^2}{10^{-7}} = 10^4 \Rightarrow l' = 100 \text{ m}$$

الجواب (B)

$$U_{\text{max}} = \frac{q_{\text{max}}}{C} = \frac{4 \times 10^{-4}}{4 \times 10^{-6}} = 100 \text{ V} \quad (11)$$

الجواب (B)

$$E = \frac{1}{2} \frac{q_{\text{max}}^2}{C} = \frac{1}{2} \frac{16 \times 10^{-8}}{4 \times 10^{-6}} \quad (12)$$

$$E = 2 \times 10^{-2} \text{ J} \quad \text{الجواب (C)}$$

$$l' = 2\pi r \times N \Rightarrow N = \frac{l'}{2\pi r}$$

$$N = \frac{18}{2\pi \times 2 \times 10^{-2}} = \frac{1800}{4\pi} = \frac{18 \times 32\pi}{4\pi}$$

$$N = 144 \text{ لف} \quad \text{الجواب (C)}$$

$$q_{\text{max}} = C \times U_{\text{max}} = 10^{-12} \times 10^3 = 10^{-9} \text{ C} \quad \text{الجواب (C)}$$

$$q_{\text{max}} = C \times U_{\text{max}} = 10^{-12} \times 10^3 = 10^{-9} \text{ C} \quad (15)$$

$$E = \frac{1}{2} \frac{q_{\text{max}}^2}{C} = \frac{1}{2} \frac{10^{-18}}{10^{-12}} = \frac{1}{2} \times 10^{-6} \text{ J} = 5 \times 10^{-7} \text{ J} \quad \text{الجواب (A)}$$

المدرس فراس قلعه جي  
 مدير في القسم الفيزيائية والكيمياء  
 في الثانوية القروي  
 98844-057

$$q_{max} = C U_{max} = 10^{-8} \times 10^2 = 10^{-6} \text{ C} \quad (9)$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-4} \times 10^{-8}}} = 10^6 \text{ rad.s}^{-1}$$

$$I_{max} = \omega_0 q_{max} = 10^6 \times 10^{-6} = 1 \text{ A}$$

$$\Rightarrow i = I_{max} \cos(\omega_0 t + \frac{\pi}{2})$$

$$i = 1 \cos(10^6 t + \frac{\pi}{2}) \quad \text{الجواب (D)}$$

$$I_{max} = \omega_0 q_{max} \quad \dots (11) \quad (10)$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \dots (2)$$

$$C = \frac{q}{U} = \frac{0.3 \times 10^{-6}}{300} = 1 \times 10^{-9} \text{ F}$$

$$L = 4\pi \times 10^{-7} \frac{N^2}{l} S$$

$$N = \frac{l'}{2\pi r} \quad S = \pi r^2 \quad \text{كأنه نفوضه:}$$

$$L = 4\pi \times 10^{-7} \frac{l'^2}{\frac{4\pi^2 r^2}{l} \pi r^2} \Rightarrow$$

$$L = \frac{10^{-7} \times l'^2}{l} = \frac{10^{-7} \times 324}{9 \times 10^{-2}}$$

$$L = 36 \times 10^{-5} \text{ H}$$

نفوضه بـ (2):

$$\omega_0 = \frac{1}{\sqrt{36 \times 10^{-5} \times 10^{-9}}} = \frac{10^7}{6}$$

$$\omega_0 = \frac{1}{6} \times 10^7 \text{ rad.s}^{-1}$$

نفوضه بـ (11):

$$I_{max} = \frac{1}{6} \times 10^7 \times 0.3 \times 10^{-6} = 0.5 \text{ A}$$

الجواب (A)

$$f_0 = \frac{1}{8\sqrt{\pi^2 \times 10^{-13}}} = \frac{1}{8} \times 10^6 = 125 \times 10^3 \text{ Hz} \quad \text{الجواب (C)}$$

$$f_0 = \frac{1}{T_0} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{10^{-6} \times 10^{-2}}} \quad (11)$$

$$f_0 = \frac{1}{2\pi} \times 10^4 = \frac{100 \times 100}{2\pi} = \frac{3.2 \pi}{2\pi} \times 100 = 1600 \text{ Hz} \quad \text{الجواب (A)}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow 10^5 = \frac{1}{\sqrt{10^{-3} C}} \quad (6)$$

نرفع الطرفين:

$$10 = \frac{1}{10^{-3} C} \Rightarrow C = 10^{-7} \text{ F}$$

$$U = \frac{q}{C} = \frac{10^{-6}}{10^{-7}} = 10 \text{ V} \quad \text{الجواب (B)}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-2} \times 10^{-8} \times 10^{-6}}} = 10^8 \text{ rad.s}^{-1} \quad \text{الجواب (A)}$$

$$T_0 = \frac{\lambda}{v} = 2\pi\sqrt{LC} \quad (11)$$

$$\frac{-66}{-3 \times 10^8} = 2\pi\sqrt{L \times 10^{-12}} \Rightarrow \text{نرفع الطرفين}$$

$$\frac{400}{10} = 40 \times L \times 10^{-12} \Rightarrow L = \frac{10^{-15}}{10^{-12}}$$

$$L = 10^{-3} \text{ H} \quad \text{الجواب (C)}$$

$$I_{max} = \omega_0 q_{max} \quad \dots (11) \quad (8)$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-4} \times 4 \times 10^{-6}}} = \frac{1}{2} \times 10^5 \text{ rad.s}^{-1}$$

$$\Rightarrow I_{max} = \frac{1}{2} \times 10^5 \times 4 \times 10^{-4} = 20 \text{ A} \quad \text{الجواب (D)}$$



٦

$$f_0 = \frac{1}{T_0} = \frac{1}{2\pi\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{10^{-2} \times 10^{-12}}} = \frac{10^7}{2\pi}$$

$$f_0 = \frac{100 \times 10^5}{2\pi} = \frac{32\pi}{2\pi} \times 10^5$$

$$f_0 = 16 \times 10^5 \text{ Hz} \quad \text{الجواب (B)}$$

$$I_{max} = \omega_0 q_{max} \quad \dots (11) \quad (16)$$

$$q_{max} = C \cdot U_{max} = 10^{-12} \times 10^3 = 10^{-9} \text{ C}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-2} \times 10^{-12}}} = 10^7 \text{ rad.s}^{-1}$$

$$\Rightarrow I_{max} = 10^7 \times 10^{-9} = 0.01 \text{ A}$$

$$\Rightarrow i = I_{max} \cos(\omega_0 t + \frac{\pi}{2})$$

$$i = 0.01 \cos(10^7 t + \frac{\pi}{2}) \quad \text{الجواب C}$$

(15)

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow 10^3 = \frac{1}{\sqrt{10^{-4}C}} \quad (11)$$

$$10^6 = \frac{1}{10^{-4}C} \Rightarrow C = \frac{1}{100} = 10^{-2} \text{ F}$$

تردد الطبيعي:

الجواب (B)

$$I_{max} = \omega_0 q_{max} = 10^3 \times 10^{-2} = 10 \text{ A} \quad (12)$$

$$i = I_{max} \cos(\omega_0 t + \frac{\pi}{2})$$

$$i = 10 \cos(10^3 t + \frac{\pi}{2}) \quad \text{الجواب (D)}$$

$$T_0 = \frac{\lambda}{v} = 2\pi\sqrt{LC} \quad (13)$$

$$\frac{\lambda}{3 \times 10^8} = 2\pi\sqrt{10^{-3} \times 10^{-12}} \Rightarrow$$

$$\lambda = 6 \times 10^8 \sqrt{\pi^2 \times 10^{-15}} = 60 \text{ m}$$

الجواب (C)

$$f_0 = \frac{1}{T_0} = \frac{1}{2\pi\sqrt{LC}} \quad \dots (14)$$

$$C = \frac{q}{U} = \frac{0.4 \times 10^{-6}}{200} = 2 \times 10^{-9} \text{ F}$$

$$L = \frac{10^{-7} \times 16^{12}}{l} \quad (\text{تم استنتاجها سابقاً})$$

$$L = \frac{10^{-7} \times 1600}{20 \times 10^{-2}} = 8 \times 10^{-4} \text{ H}$$

$$f_0 = \frac{1}{2\pi\sqrt{8 \times 10^{-4} \times 2 \times 10^{-9}}} = \frac{1}{8\sqrt{\pi^2 \times 10^{-13}}} \quad \text{نقوضه بـ (A):}$$

$$f_0 = \frac{10^6}{8} = 125 \times 10^3 \text{ Hz}$$

الجواب (A)

المدرس فراس قلعه جي  
إجازة في العلوم الفيزيائية والتكنولوجيا  
معلوم في التواصل الإلكتروني  
380-337760  
088440574