



EE 202 – CIRCUIT THEORY II

MID TERM LAB EXAM

Grade

99/100

Name, Family Name:

ID No.: [REDACTED] 1033

Instructions:

- Write your student ID number on the top of each page.
- Show all the details of your analysis and calculations on the blank page provided with this exam paper.

Q1. Draw the circuit using Multisim using the Figure below, and record the values in the given Table. Use the potentiometer ($2\text{ k}\Omega$) at minimum position, and use $10\text{ k}\Omega$ resistors as Load resistors. [CO_4, PI_2_16, SO_2]

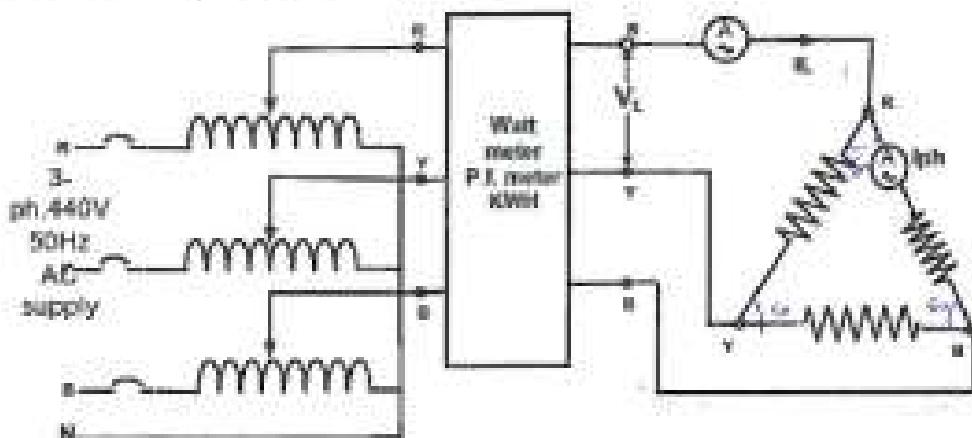


Figure 1

No.	Line Voltage V_L (Volts)	Line Current I_L (Amp)	Phase Current I_P (Amp)	Ratio of Line to Phase Current (I_L / I_P)	Power By Calculation $W = 1.73 \cdot V_L \cdot I_L \cdot \cos \theta + j \cdot \frac{V_L}{I_P} \cdot I_P^2$ (Watts)	Power Calculation (Exp) (Watts)
190, 523	110	19.53A	19.53A	1.732	5.938 W	5.445 W
381, 688	220	66.67A	38.105A	1.732	21.754 W	21.281 W
762161	440	131.34A	76.215A	1.732	87.030 W	82.182 W

TABLE 1 (Delta Connected Load)

Sorry for that


Q4. Draw square waveform, and show a) peak value b) peak to peak value, and c) time period on the waveform

- peak value



it's +2 or -2

- peak to peak


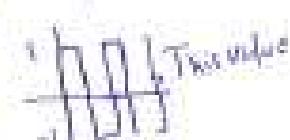


it's 4 from -2 to +2

- Time period

it's one period and it's

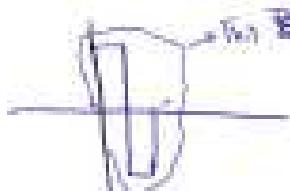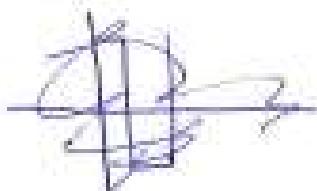~~peak~~ 2 peak value ~~width~~ so ~~width~~ peak + peak




~~for~~ ~~time period~~

Q5. What is the relationship of the inductive and capacitive reactance with frequency?

It's direct proportion in inductive with Frequency
so when the frequency increase the inductive
will be increase also

It's reverse proportion in capacitive with Frequency
so when the frequency increase the ~~and~~ capacitive
will be decrease

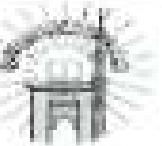

EE 202 – CIRCUIT THEORY II

Spring Semester 2016-2017

MIDTERM LAB EXAM

GRADING TABLE

Section No.: 1053

Name, Family Name: [REDACTED]

[CO_4, PI_2_16, SO_2]

Contents	Grade	Comments
Q1		
Circuit Wiring	15/25	
Circuit Functioning	15/15	
Line Voltage (measurement)	5/05	
Line Current (measurement)	5/05	
Phase Current (measurement)	5/05	
Power (measurement)	10/10	
Power (Calculation)	10/10	
Q2	1/05	
Q3	5/05	
Q4	9/10	
Q5	5/05	
Total	57 /100	

Instructor Full Name	Nathirulla Sheriff
Signature	
Date	02-11-2017

Calculations

$$w = 1.73 \times 19.529 \times 33.001 \times 10^3 \text{ rad/s} \cos(60^\circ) = 105.438 \text{ rad/s}$$

$$w = 1.73 \times 381.058 \times 66.001 \times 10^3 \text{ rad/s} \cos(60^\circ) = 21.754 \text{ rad/s}$$

Ratio $\frac{I_L}{I_{ph}} = \frac{33.001}{19.529} = 1.732 \text{ mP}$

$$\frac{I_L}{I_{ph}} = \frac{66.001}{38.105} = 1.732 \text{ mP}$$

Q2. What is the relation between the phase and line current based on the Multisim workbench results?

The relation between I_L And I_{ph} is

$I_L = \sqrt{3} I_{ph}$ in Y to ~~Δ~~ Δ

And $I_L = I_{ph}$ in Y to Y



Q3. Do we get similar relation between line voltage and the corresponding phase voltage if the load is star connected?

~~Yes in Y to Δ connected and No in Y to Y~~

~~$V_L = \sqrt{3} V_{ph}$ in Y to Δ~~

~~$V_L = V_{ph}$ in Y to Y~~