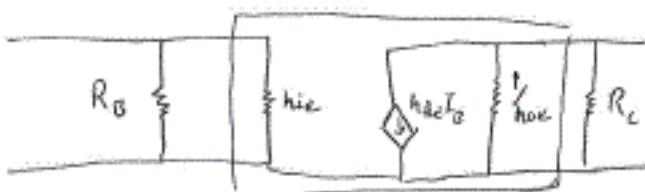


Question 3 (10 points)

Make a hybrid small signal equivalent model and find

- Input Impedance
- Output Impedance
- Voltage gain

Solution




$$Z_i = R_B \parallel h_{ie} = \frac{(330k)(1.17k)}{(330k) + (1.17k)} = 1165.87 \Omega$$

$$Z_o = \frac{1}{h_{oc}} \parallel R_C = \frac{(50k)(2.7k)}{(50k) + (2.7k)} = 2561.67 \Omega \quad \approx R_C$$

~~$$A_v = \frac{V_o}{V_i}$$~~

$$A_v = \frac{-R_C (h_{fe})}{r_e}$$
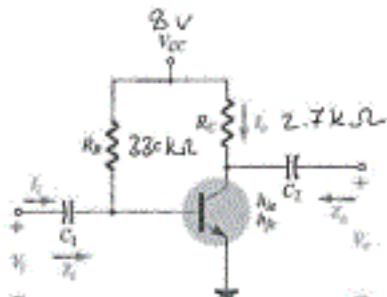
$$A_v = \frac{-Z_o}{r_e} = \frac{-2561.67}{9.75} = -262.73$$



$$h_{fe} = 120 = \beta$$

$$h_{ie} = 1.17 \text{ k}\Omega = \beta r_e$$

$$h_{oc} = 2 \text{ mA/V}$$

$$\frac{1}{h_{oc}} = 50 \text{ k}\Omega = r_o$$

$$1.17 \text{ k}\Omega = 120 r_e$$

$$r_e = \frac{1.17 \text{ k}}{120} = 9.75 \Omega$$

Question 2 (100 points)

For Emitter bias configuration, derive the expression for

Z_i

Z_0

A_v

Solution

~~$Z_A = \beta(r_e + R_E(\beta + 1))$~~

~~EBZ~~

$$Z_A = \beta r_e + R_E(\beta + 1)$$

$$= \beta(r_e + R_E)$$

$$\therefore Z_i = Z_A \parallel R_B$$

$$Z_o = R_C \quad \checkmark$$





$$A_v = \frac{-V_o}{V_i} = \frac{-R_C}{R_E}$$

\checkmark

(4)

\checkmark

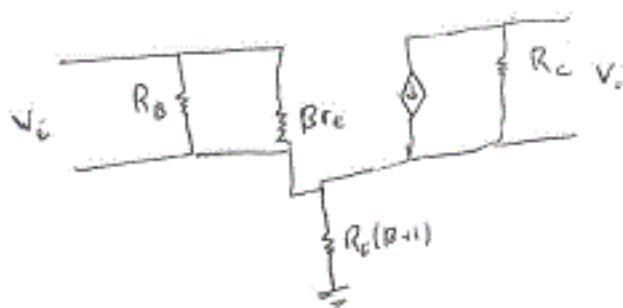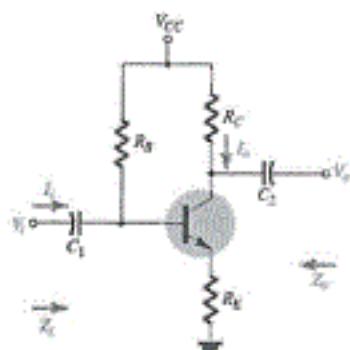

Question 1 (10 points)

For voltage divider bias configuration, find the following. Take r_o as $50\text{k}\Omega$. Draw the r_e small signal equivalent model and find

r_e

Z_i

Z_o

A_v

Solution

$$r_e = \frac{26m}{I_E}$$


~~$R_{Th} = 56k \parallel 8.2k = 4.60.87\text{ }\Omega$~~

$$R_{Th} = \frac{56k \times 8.2k}{56k + 8.2k} = 7152.65 \Omega \quad V_{Th} = 2.81 \text{ V} = V_B$$

$$\therefore V_{BE} = V_B - V_E \Rightarrow 0.7 = 2.81 - V_E \quad \boxed{\therefore V_E = 2.11 \text{ V}}$$

$$\therefore I_E = \frac{2.11}{1.5k} = 1.407 \text{ mA}$$
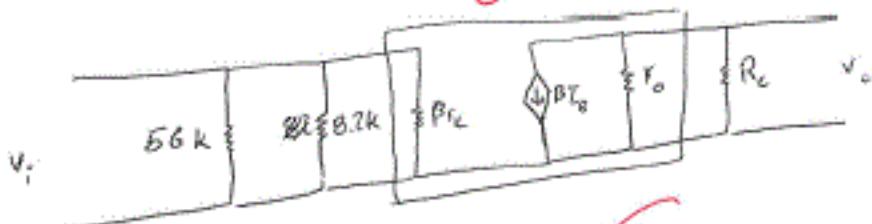
$$\checkmark r_e = \frac{26m}{1.407m} = 18.479 \Omega$$



(1+)

$$Z_i = R_{Th} \parallel \beta r_e = \frac{7152.65 \times (90)(18.479)}{7152.65 + (90)(18.479)} = 1349.36 \Omega$$

$$Z_o = R_c \parallel r_o = \frac{(6.8k)(50k)}{(6.8k) + (50k)} = 5985.91 \Omega$$

$$A_v = -\frac{R_c \parallel r_o}{r_e} = \frac{-5985.91}{18.479} = -323.93 \text{ V}$$



EE 212 - ELECTRONICS II

Fall Semester 2016-2017

Midterm Exam 2

Exam Date: December 12, 2017; Exam Duration: 70 minutes

Student's Full Name: _____

Student ID #: _____ Section #: 1050 Signature: _____

Instructions:

- Write your student ID number on the top of each page
- Write the solution in the space provided under each question
- Show all the details of your analysis and calculations

Question No.	Points Assigned	Points Awarded
3. [CO_7, PI_5_53, SO_5]	10	10
4. [CO_7, PI_5_53, SO_5]	10	4
5. [CO_7, PI_5_53, SO_5]	10	9
Total	30	23

Instructor's Full Name	Dr. Abdul Waheed Malik
Signature	