

Student ID #: _____

not clear how
to calculate?

I_B (calculated)	18.82 μ A
I_C (calculated)	6.42 mA
β (calculated)	340.55
V_B (measured)	0.556 V
V_C (measured)	2.709 V
V_{CE} (measured)	2.705 V
V_B (calculated)	0.7 V
V_C (calculated)	7.68 V
V_{CE} (calculated)	2.67 V
% error V_B	4.8%
% error V_C	1.97%
% error V_{CE}	0.98%

10. Compare and comment about the discrepancies in the measured and calculated values of

V_B , V_C and V_{CE} based on % error. it's have some different between And

The value of calculate it's more accurate than measured

Because we use ideal thing but in measured the component it's not ideal

11. Which is more stable biasing circuit, common emitter or voltage divider? Comment.

Voltage divider is more stable because it's more useful

in our life and we can use in different ways in our life

because voltage divider make part clear

CALCULATIONS

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = 18.82 \mu A$$

$$I_C = (\beta + 1) I_B$$

$$I_C = \frac{V_C}{R_C} = 6.42 \times 10^{-3}$$

$$\beta = \frac{I_C}{I_B} = 340.55$$

$V_{CE} = ?$

V_B it's a diode

$$V_C = V_{CC} - V_{R_C} = 2.68 V$$

$$\text{or } V_C = V_{CE} \approx 2.68$$

$$V_{CE} = V_C - V_B = V_C = 2.68$$

not clear
details



EE 212 - ELECTRONICS I

Fall Semester 2017

LAB FINAL EXAM

Grade

Name, Family Name: _____

ID: _____ Section No.: 1050 Signature: _____

[CO_12, PI_2_35, SO_2]

Instructions:

- Write your student ID number on the top of each page.
- Show all the details of your analysis and calculations.

1. Consider the circuit shown in Figure 1. Let $R_C = 2.7 \text{ k}\Omega$, $R_B = 1 \text{ M}\Omega$.
2. Measure and record each resistor value in Table 1.
3. Measure the voltages V_{BE} , V_{RC} and record them in Table 1.
4. Calculate the voltages of V_{BE} , V_{RC} and record the values in Table 1.
5. Calculate the currents I_B , I_C and record the values in Table 1.
6. Calculate the β and record the value in Table 1.
7. Measure the voltages V_B , V_C and V_{CE} , and record the values in Table 1.
8. Calculate the voltages V_B , V_C and V_{CE} , and record the values in Table 1.
9. Calculate the % error between the measured and calculated values of V_B , V_C and V_{CE} and record them in Table 1.

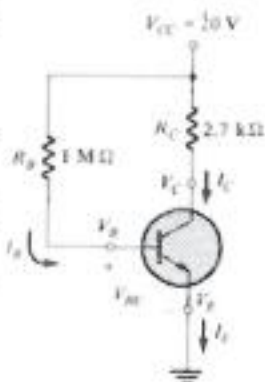


Figure 1

Table 1

Parameter	Values
R_C (measured)	2.661 kΩ
R_B (measured)	1.023 MΩ
V_{BE} (measured)	0.666 V
V_{RC} (measured)	17.372 V
V_{BE} (calculated)	0.7 V
V_{RC} (calculated)	17.36 V

? how?



EE 212 - ELECTRONICS I

Fall Semester 2017

LAB FINAL EXAM

GRADING TABLE

Section No.: 1050

Name, Family Name: [REDACTED]

[CO_12, PI_2_35, SO_2]

Contents	Grade	Comments
Circuit connections	12 /12	
Circuit Functioning	12 /12	
R_C (measured)	4 /4	
R_B (measured)	4 /4	
V_{BE} (measured)	4 /4	
V_{RC} (measured)	4 /4	
V_{BE} (calculated)	3 /3	
V_{RC} (calculated)	3/0 /3	
I_B (calculated)	3 /3	
I_C (calculated)	1 /3	
β (calculated)	4 /4	
V_B (measured)	4 /4	
V_C (measured)	4 /4	
V_{CE} (measured)	4 /4	
V_B (calculated)	3 /3	
V_C (calculated)	3 /3	
V_{CE} (calculated)	3 /3	
% error V_B	3 /3	
% error V_C	3 /3	
% error V_{CE}	3 /3	
Analysis	04 /8	
Calculation details	04 /6	
Total	89 /100	