

The major goals of this chapter are to enable you to:

1. Describe the nature of electric charges.
2. Distinguish conduction and induction.
3. Use Coulomb's law to find the force between charges.
4. Describe the characteristics of electricity.
5. Use Ohm's law to solve electric flow problems.
6. Use electrical symbols to describe circuits.
7. Find current, voltage, and resistance in simple circuits.
8. Describe the nature of cells and batteries.
9. Analyze circuits with cells in series and parallel.
10. Find electric power.

# Electricity

• Electricity is the name given to a wide range of electrical phenomena, such as

- lightning.

- spark when we strike a match.

- what holds atoms together.

- \* المطرية بـ إسـمـةـ تـلـفـاعـ مـنـ مـاءـ
- \* المـطـلـقـ الـهـرـاـكـ مـدـيـ وـاسـعـ مـنـ
- \* الـمـدـيـ الـهـرـاـكـ مـدـيـ مـدـيـ
- \* الـمـدـيـ الـهـرـاـكـ مـدـيـ مـدـيـ

• Electrostatics involves electric charges,

- the forces between them,
- the aura that surrounds them, and
- their behavior in materials.



Hasta

Hasta

at all - lose,

Scoring

(1)

# Electric Force and Charges

القواعد

القواعد

القواعد

Central rule of electricity

القواعد

- Opposite charges attract one another;
- Like charges repel.


الدوري

الواحدة

الدوري

الواحدة

الدوري

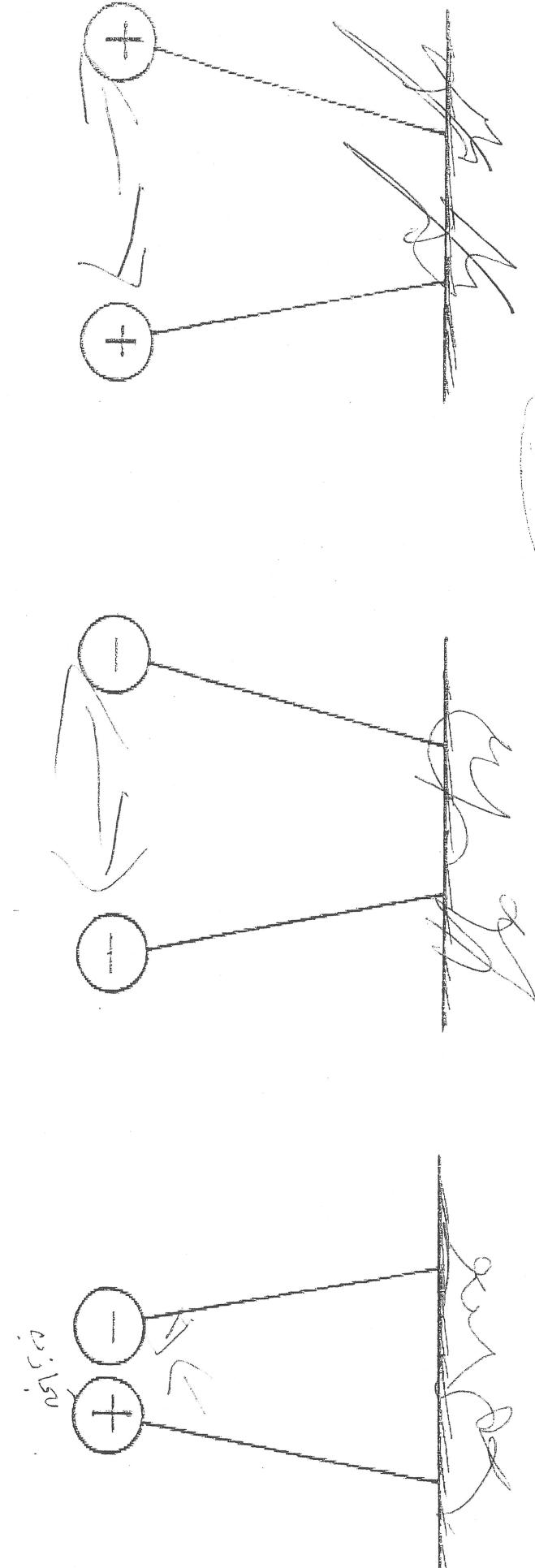

# Electric Force and Charges

الملحوظة

الملحوظة

الملحوظة

الملحوظة

## ① Protons

- Positive electric charges

- Repel positives, but attract negatives


## ② Electrons

- Negative electric charges

- Repel negatives, but attract positives

## ③ Neutrons

- Neutral electric charge

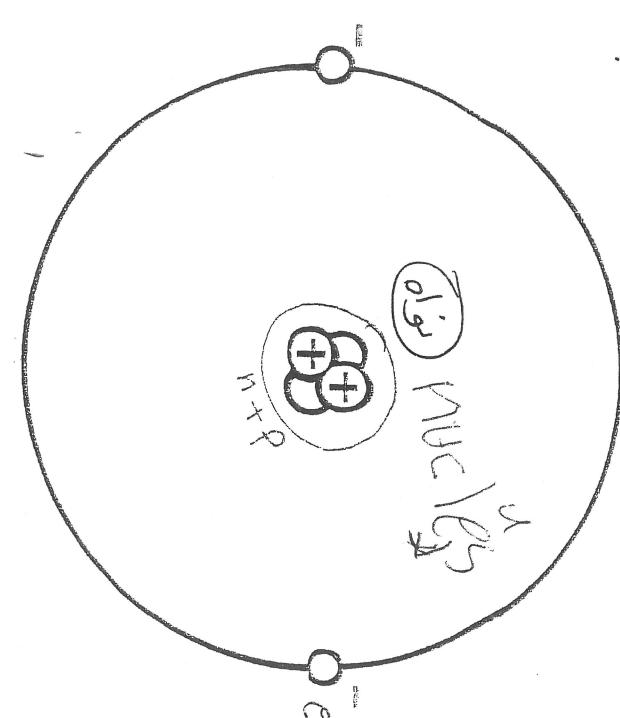

(P)

# Electric Force and Charges

الكترونيات

الكترونيات

الكترونيات

## Fundamental facts about atoms

1. Every atom is composed of a positively charged nucleus surrounded by negatively charged electrons.

2. Each of the electrons in any atom has the same quantity of negative charge and the same mass.

$$m_n > m_e > m_p$$

- ① كل ذرة مكونة من نواة موجبة المقدار ومحاطة بذرة سالبة المقدار.
- ② ذرات الذكرولات هي ذرات دافعة لها فرقة إيجابية، ومن الممكن إدخالها في الماء.
- ③ البروتونات والبيرونات تؤلف النواة، حيث يترك كلاً منها البروتونات.
- بروتون: كتلته النترون أكثر تقليلًا من كتلة البروتون، وبذلك له وزن أقل.

- ④ الهرة مادة ممدوحة على عدد بروتوناته عدد الذكرولات.

Y

# Electric Force and Charges

الكترونات  
الموجة

العنصر  
الموجة

## Fundamental facts about atoms (continued)

3. Protons and neutrons compose the nucleus. Protons are about 1800 times more massive than electrons, but each one carries an amount of positive charge equal to the negative charge of electrons. Neutrons have slightly more mass than protons and have no net charge.
4. Atoms usually have as many electrons as protons, so the atom has zero net charge.

البروتونات والنيترونات لهما 1800 مرتين كثافة الكهرباء  
وتحلقي ولذلك مقدار حمله اليدوي يساوى صفر سنت اللكترونات

مقدار الكهرباء



ومن بين كل هذه المقادير

# Electric Force and Charges

الكتروستاتيك

الكترو

الكتروني

Ion

أيون

Positive ion – atom losing one or more electrons has positive net charge.

أيون إيجي

إيجي

Negative ion – atom gaining one or more electrons has negative net charge.

أيون سالب

سالب

- \* الديون الموجبة: دُسّة نشطة قادر على اكتraction و repulsion electrons other than its own.
- \* الديون السالبة: دُسّة نشطة قادر على جذب electrons other than its own.

# Electric Force and Charges

القوى الكهربائية

الإيجاد

## Electrons in an atom

الإلكترونات

الإلكترون

- Innermost – attracted very strongly to oppositely charged atomic nucleus
- Outermost – attracted loosely and can be easily dislodged

إيجاد

إيجاد

إيجاد

إيجاد

الإيجاد

الإيجاد

# Electric Force and Charges

## Electrons in an atom

### Examples:


- When rubbing a comb through your hair, electrons transfer from your hair to the comb. Your hair has a deficiency of electrons (positively charged).
- When rubbing a glass rod with silk, electrons transfer from the rod onto the silk and the rod becomes positively charged.

الكتل الكهربائية تأتي من الماء. فإذا تم بذل جهد على ماء الكهرباء، فسوف تأتي الكتلة الكهربائية من الماء. فإذا تم بذل جهد على الماء، فسوف تأتي الكتلة الكهربائية من الماء.

~~Coulomb's law~~
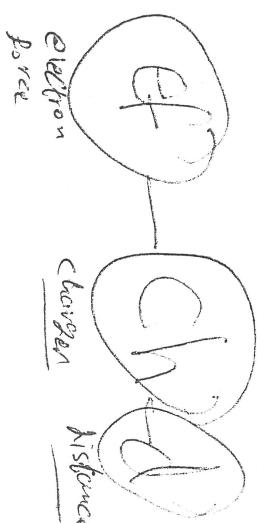
## Coulomb's Law

القانون الكهربائي هو قانون يربط بين القوى الكهربائية المعاين



قانون

### Coulomb's law

- Relationship among electrical force, charge, and distance

discovered by Charles Coulomb in the 18th century

- States that for a pair of charged objects ( $q_1$  and  $q_2$ ) that are much smaller than the distance ( $d$ ) between them,
- { the force between them varies directly, as the product of their charges, and inversely, as the square of the separation distance }

\* لمحظى مارتن كولوم

- ① المؤنة بين المتناسب مع مجموع المقادير المقابلة.
- ② تتناسب مع مجموع المقادير المقابلة.

(1)

$F \propto q_1 q_2$

$$F \propto \frac{q_1 q_2}{d^2}$$

(2)

# Coulomb's Law

## Coulomb's law (continued)

- If the charges are alike in sign, the force is repelling; if the charges are not alike, the force is attractive.

- In equation form:

$$F = k \frac{q_1 q_2}{d^2}$$

الแรง الكهربائي  
المسافة بين المقطفين  
مربع

$$k = 9,000,000,000 \text{ Nm}^2/\text{C}^2$$

عدد كارل كولوم: نسبة معاين للكثافة الكهربائية

- Similar to Newton's law of gravitation for masses

- Underlies the bonding forces between molecules

$$F \propto \frac{1}{r^2}$$

(inversely proportional)

$$F \propto \frac{1}{r^2}$$

(inversely proportional)

\* مماثلة للجاذبية في سبي الكواكب بين مرمياتها

(5)

# Electric Field

on electric field

مجال

(أيضاً مجال جذب أو جذب)

①

Electric field

مجال

• Space surrounding an electric charge (an energetic aura)

describes electric force

جذب جذب

• Around a charged particle obeys inverse-square law

Force per unit charge (unit:  $\text{N/C}$ )



$$F = \frac{q}{r^2}$$

If a body with charge  $q$  experiences a force  $F$  at some point in space, then the electric field  $E$  at that point is

$$E = \frac{F}{q}$$

\* ولكن يجب أن يكون في مفهوم مقدار المقدار

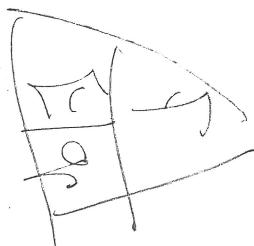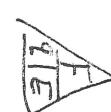اللهم لا يجوز له أن تسمى بـ electric field



# Electric Field



المجال الكهربائي

\* تكون المقادير المطلوبة متساوية  
\* كذا المقدار المطلوب يساوى المقدار المطلوب
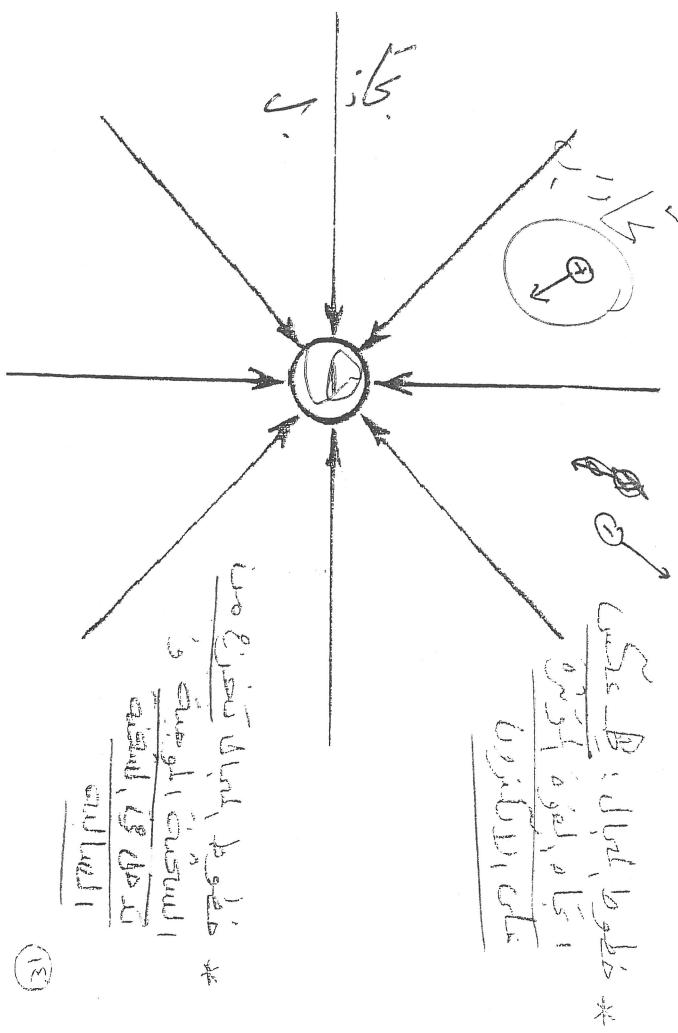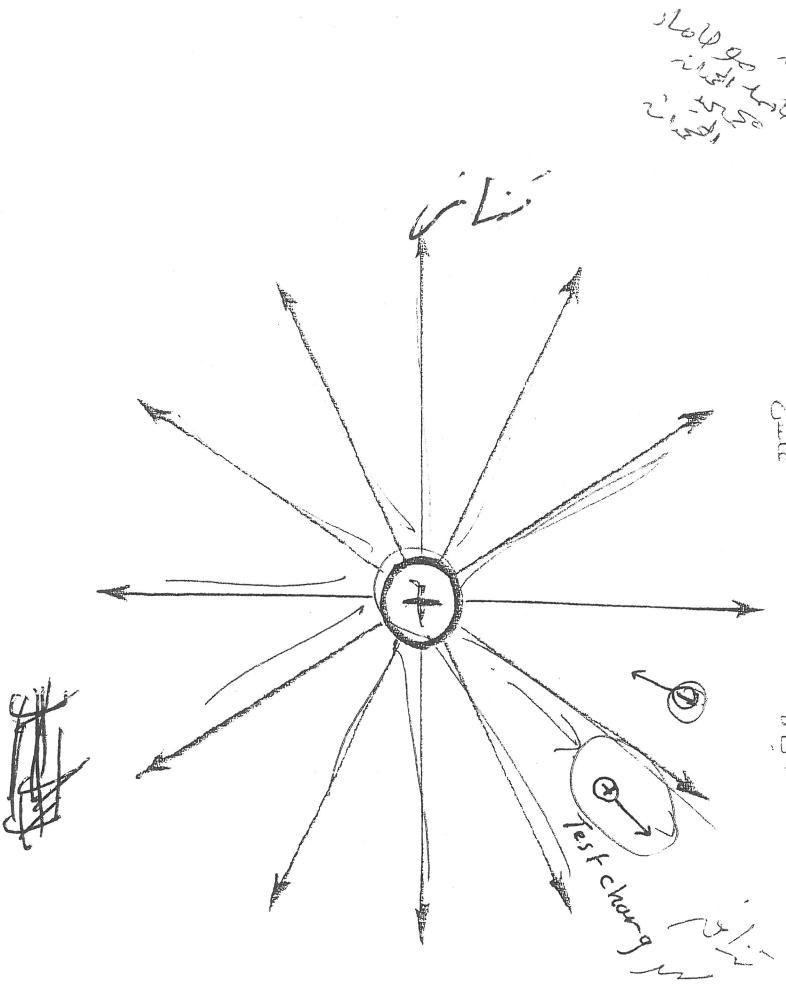
## Electric field direction

• Same direction as the force on a small positive test charge

• Opposite direction to the force on an electron



$$6.50 \times 10^{-6}$$

$$\mu = 10^{-6}$$

## EXAMPLE 4

Two charges each with magnitude +6.50  $\mu C$ , are separated by a distance of 0.200 cm.

Find the force of repulsion between them.

$$0.200 = 2 \times 10^{-3} \text{ m}$$

Data:

$$q_1 = q_2 = +6.50 \mu C = +6.50 \times 10^{-6} C$$

$$r = 0.200 \text{ cm} = 0.00200 \text{ m} = 2.00 \times 10^{-3} \text{ m}$$

$$k = 9.00 \times 10^9 \text{ N m}^2/\text{C}^2$$

$$F = ?$$

Basic Equation:

$$F = \frac{kq_1q_2}{r^2}$$

Working Equation: Same

$$F = \frac{(9.00 \times 10^9 \text{ N m}^2/\text{C}^2)(6.50 \times 10^{-6} \text{ C})(6.50 \times 10^{-6} \text{ C})}{(2.00 \times 10^{-3} \text{ m})^2}$$

$$= 9.51 \times 10^4 \text{ N}$$

Substitution:


# Some electric field configurations.

الطبعة الأولى

المجلد الأول


الكتاب السادس / شركات طباعة

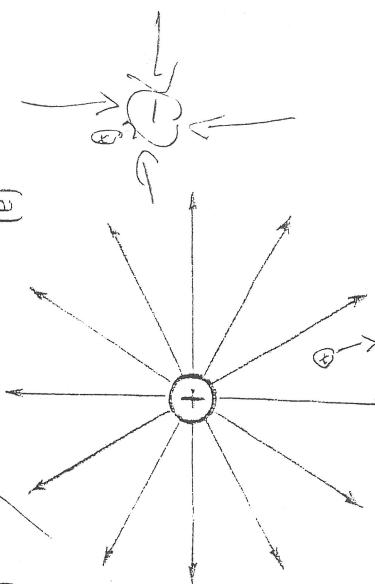(a) Lines of force emanating from a single positively charged particle.



(a)

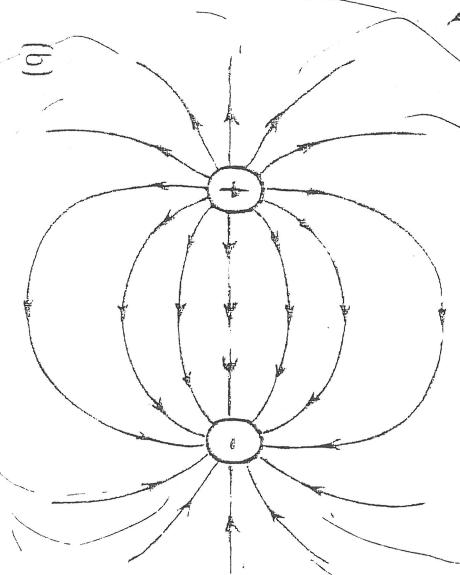
(b) Lines of force for a pair of equal but oppositely charged particles. Note that the lines emanate from the positive particle and terminate on the negative particle.



(b)

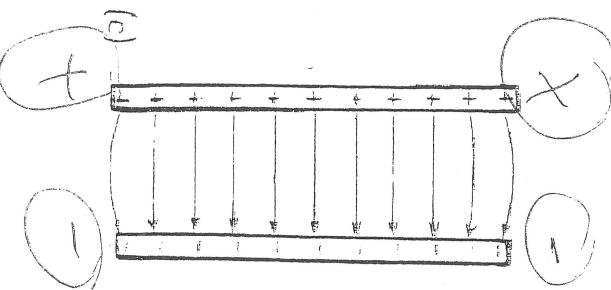(c) Uniform lines of force between two oppositely charged parallel plates.

كتاب السادس / شركات طباعة  
الطبعة الأولى / شركات طباعة  
الكتاب السادس / شركات طباعة




(c)

# Electric Potential

الجهد الكهربائي
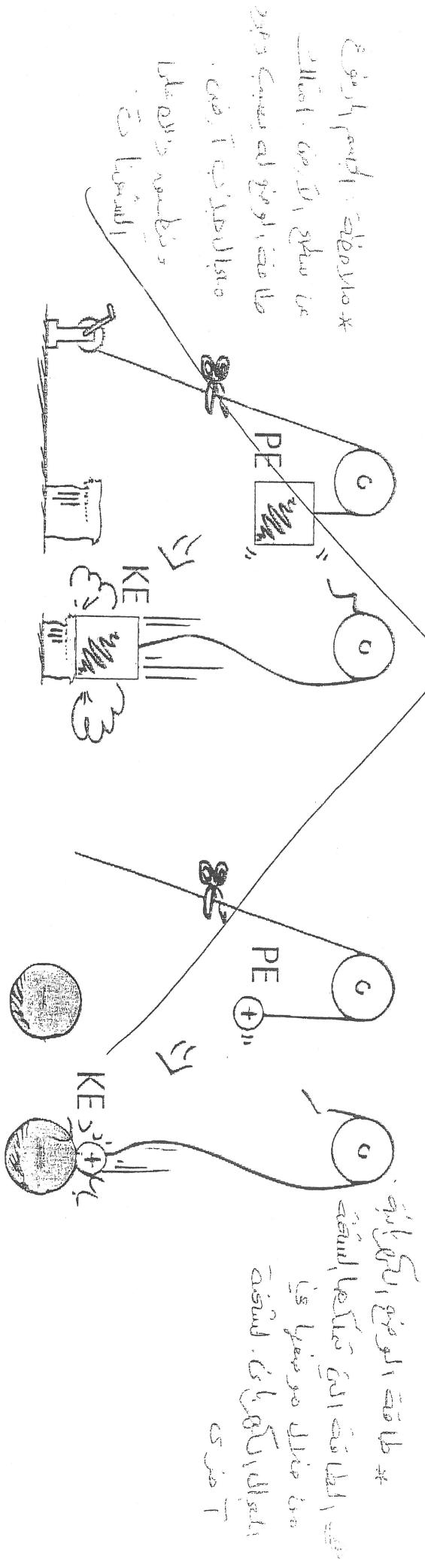
## Electric potential energy (unit: Joule (J))

- Energy possessed by a charged particle due to its location in an electric field. Work is required to push a charged particle against the electric field of a charged body.




# Electric Potential


الطاقة الكهربائية

الطاقة

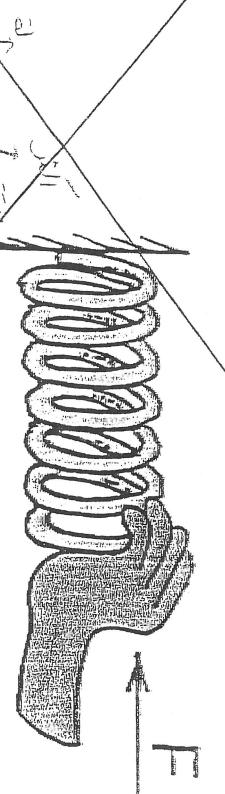الطاقة الكهربائية تختلف باختلاف  
الظروف المحيطة



a

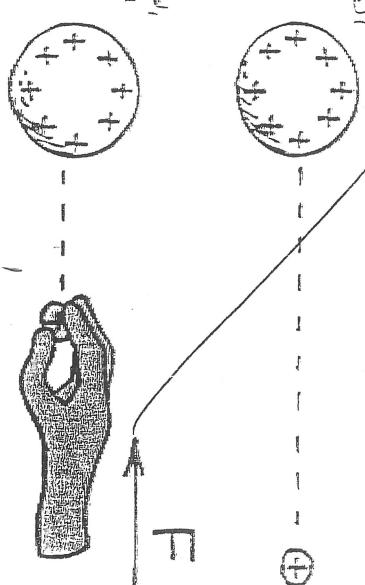

b


- (a) The spring has more elastic PE when compressed. (b) The small charge similarly has more PE when pushed closer to the charged sphere. In both cases, the increased PE is the result of work input.

• مقدار

$\Theta_{2c}$

## Electric Potential


الرمان

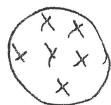

الجذب

الجاذبية  
الجاذبية

Electric potential (voltage)

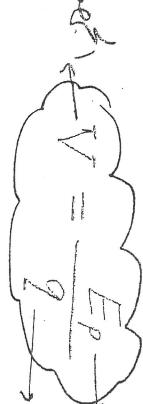\*  $V = \frac{E_p}{q}$  

Energy per charge possessed by a charged particle due to its location

مقدار

unit ( Joule )

• May be called voltage = potential energy per charge

الطاقة / الطاقة

In equation form:

مقدار


نسل

Electric potential =

electric potential/energy  $E_p$   
amount of charge ( $q$ )

الطاقة

الطاقة

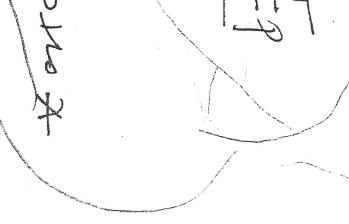[V] =  $E_p / q$  

V - Volt

J/C

( Volt ) ( جول / كيلو متر )

( J/C )


# Electric Potential

## Electric potential (voltage) (continued)

- Unit of measurement: volt,  $1 \text{ volt} = \frac{1 \text{ joule}}{1 \text{ coulomb}}$

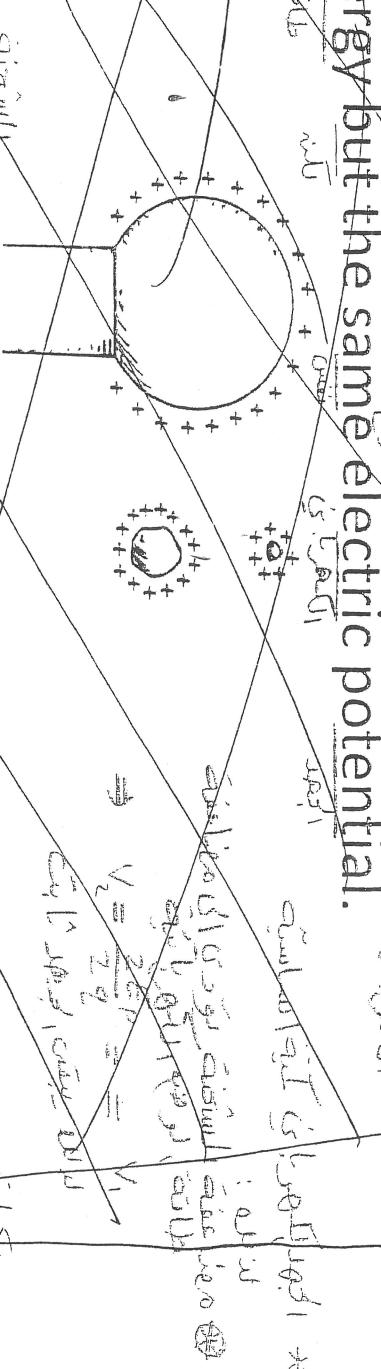Example:

- Twice the charge in same location has twice the electric potential.



- 3 times the charge in same location has 3 times the electric potential energy but the same electric potential ( $2E/2q = 3E/3q$ )

$$q = V$$

## Electric Potential

### CHECK YOUR NEIGHBOR

Color

Orange  
Orange

Electric potential energy is measured in joules. Electric potential, on the other hand (electric potential energy per charge), is measured

$$\text{J/C}$$

- A. in volts.
- B. in watts.
- C. in amperes.
- D. also in joules.

$$V = \frac{E_p}{q}$$

$$V = \frac{J}{C} \equiv V$$

$$V = \frac{J}{C}$$


## Electric Potential CHECK YOUR ANSWER

Electric potential energy is measured in joules. Electric potential, on the other hand (electric potential energy per charge), is measured

- A. in volts.
- B. in watts.
- C. in amperes.
- D. also in joules.
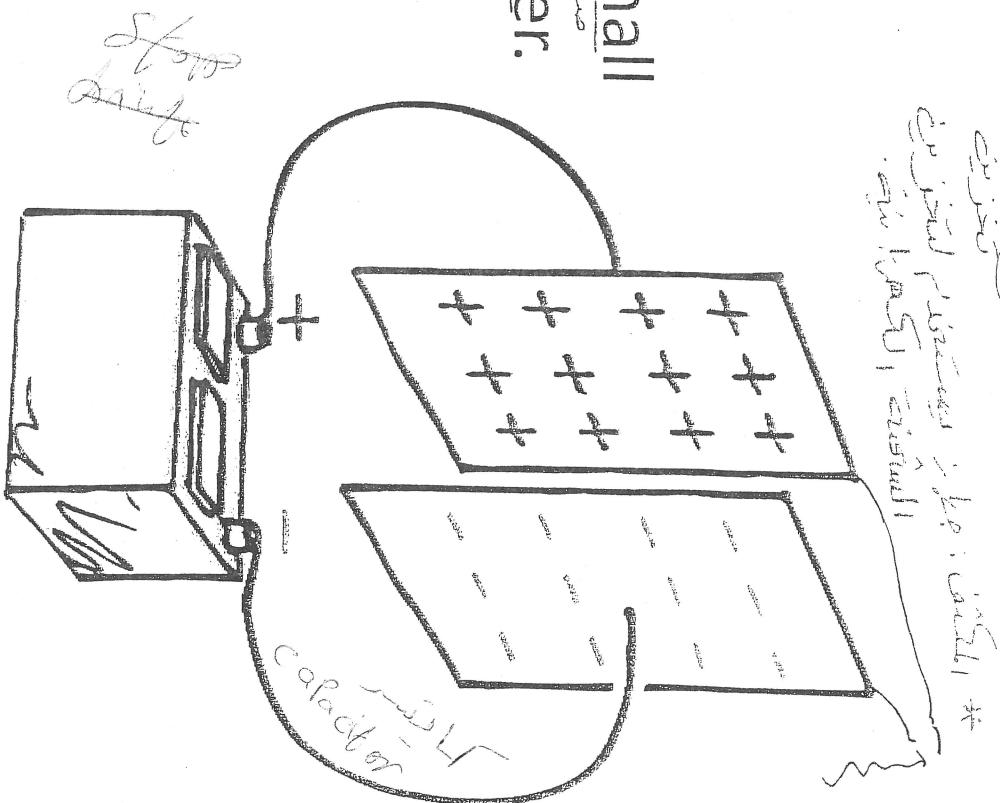
# Electric Energy Storage

- Electrical energy can be stored in a common device called a **capacitor**.
- The simplest capacitor is a pair of conducting plates separated by a small distance, but not touching each other.
- When the plates are connected to a charging device, such as the battery, electrons are transferred from one plate to the other.



ابعاد المكثف يبلغ عرضه ٣ سم وارتفاعه ٢ سم . مساحة كل من الالواح ١٠ سم مربع . على كل الالواح تأثير متساوٍ مثل المطرفة . على كل الالواح تأثير متساوٍ مثل المطرفة . مساحة كل من الالواح ١٠ سم مربع . على كل الالواح تأثير متساوٍ مثل المطرفة . على كل الالواح تأثير متساوٍ مثل المطرفة .

Conductor

Dielectric

e.g. metal

Plate

Cap

لـ (Capacitor)  
Conductor  
Dielectric

# Electric Energy Storage

- This occurs as the positive battery terminal pulls electrons from the plate connected to it.

These electrons, in effect, are pumped through the battery and through the negative terminal to the opposite plate.

- The capacitor plates then have equal and opposite charges:
  - The positive plate connected to the positive battery terminal, and
  - The negative plate connected to the negative terminal.

Electrostatic force  $\rightarrow$  Potential difference  $\rightarrow$  Potential drop  $\rightarrow$  Voltage  $\rightarrow$  Work done  $\rightarrow$  Energy stored

الله اعلم

رسورسي: في سرعة سهولة سرعة (25).  
موديل: موديل المقاومات (25).



## Electric Current

التيار

$$I = \frac{\Delta Q}{\Delta t}$$

المدة

التيار

Rate of electric flow

Measured in ampere (1 coulomb

of charge per second).


Speed of electrons (drift speed)

through a wire is slow because  
of continuous bumping of  
electrons in wire.

charge flows through a circuit,  
voltage is established across a  
circuit.

التيار

(b) Poor conductor

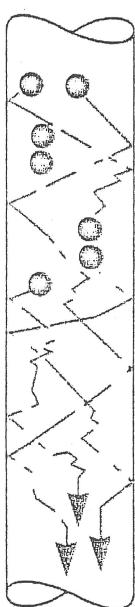

(a) Good conductor



$$C = \frac{Q}{V}$$

نحو ١٠٪

التيار

(a) Good conductor

التيار

# VOLTAGE

التي تعيّن الفرق بين طورين مختلفين في المكان، حيث يزيد طوراً عن الآخر.

The potential difference between two points in an electric field is the work done per unit of charge as the charge is moved between two points. That is,

$$\text{potential difference} = \frac{\text{work}}{\text{charge}}$$

$$V = \frac{W}{q}$$

In ~~squares~~, the raising of the potential energy of electrons that results in a potential difference across a square is called emf ( $E$ ). In circuits, the lowering of the potential difference across a load is called voltage drop.

The volt ( $V$ ), named after Alessandro Volta, is the unit of both emf and voltage drop. We define the volt as the potential difference between two points if 1 J of work is produced or used in moving 1 C of charge from one point to another.

$$1 \text{ volt (V)} = \frac{1 \text{ joule (J)}}{1 \text{ coulomb (C)}}$$

\* في كل رياضي: هنا (هذا) لطافة  
\* المؤسسة الفيدرالية للطاقة  
\* المؤسسة الفيدرالية للطاقة

في المدورة (التي) فإن الجهد يكمل

لـ (التي) المدورة (التي) تحيط بالجهاز.

\* يمتد (التي) المدورة (التي) تحيط بالجهاز.

# R E S I S T A N C E

29/1

The opposition to current flow is called resistance. The unit of resistance is the ohm ( $\Omega$ ).


The resistance of a wire depends mainly on its length ( $L$ ), cross-sectional area ( $A$ ) and a property of the material called resistivity.

These factors are related by the equation

$$R = \rho \frac{L}{A}$$

Where  
 resistivity  
 length  
 resistivity  
 resistance

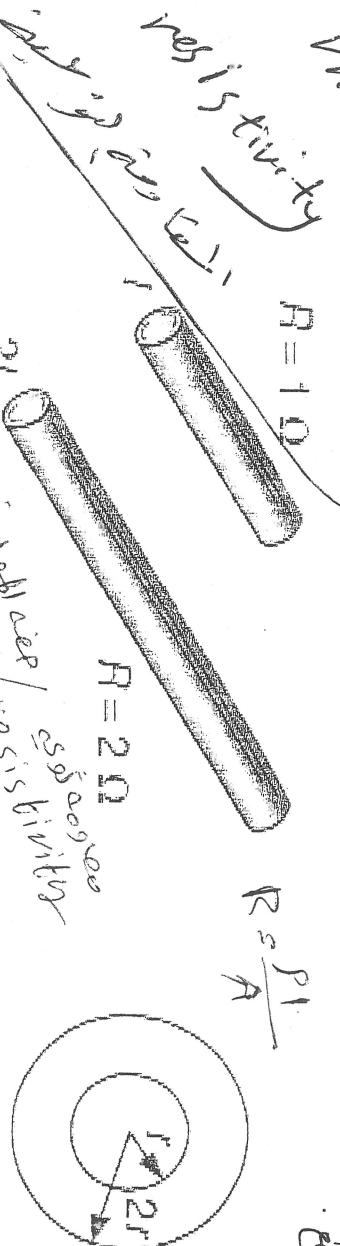- (1) Resistivity is the material property.
- (2) Length ( $L$ ) is the dimension of the wire.
- (3) Cross-sectional area ( $A$ ) is the area of a transverse section of the wire.




$$\rho = \Omega \cdot m$$

resistivity  
 length  
 resistivity  
 resistance

$\rho = \sigma \cdot m$

$$R = \sigma \frac{A}{L}$$

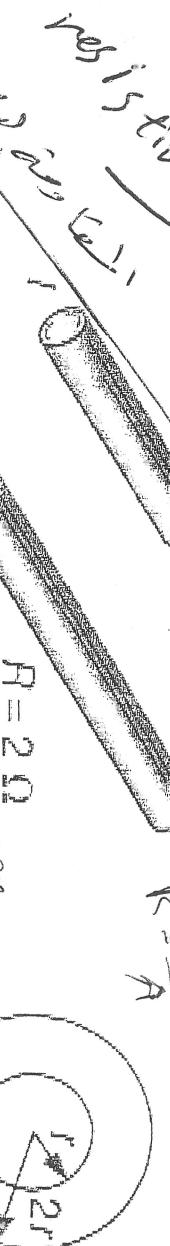

(a) Resistance varies directly with length.

(b) Doubling the radius more than doubles the cross-sectional area.

$$A = \pi r^2$$

$$A = \pi (2r)^2$$

Resistivity  $\rho$  is constant for a given material.

$$R = \rho \frac{L}{A}$$

## EXAMPLE 4.2

Find the resistance of a copper wire 20.0 m long with cross-sectional area of  $6.56 \times 10^{-3} \text{ cm}^2$  at  $20^\circ\text{C}$ . The resistivity of copper at  $20^\circ\text{C}$  is  $1.72 \times 10^{-6} \Omega \text{ cm}$ .

A

Data:

$$l = 20.0 \text{ m} = 2.00 \cancel{\text{km}}$$

$$A = 6.56 \times 10^{-3} \text{ cm}^2$$

$$\rho = 1.72 \times 10^{-6} \Omega \text{ cm}$$

$$R = ?$$

Basic Equation:

$$R = \frac{\rho l}{A}$$

Working Equation: Same

Substitution:

$$R = \frac{(1.72 \times 10^{-6} \Omega \text{ cm})(2.00 \times 10^3 \text{ cm})}{6.56 \times 10^{-3} \text{ cm}^2}$$

$$= 0.524 \Omega$$

$$R = \frac{\rho l}{A}$$

Good

①

# Ohm's Law

Ohm's law

is

دیگر مفهومی نیست بلکه این ایجاد کننده

ایجاد کننده مفهومی نیست بلکه این ایجاد کننده

$$(A) I = \frac{V}{R}$$

$$I = \frac{V}{R}$$

where  $I$  = current through the resistance

$V$  = voltage drop across the resistance

$R$  = resistance

Ohm's law can also be written

$$R = \frac{V}{I}$$

$$V = IR$$

Where  $E$  = emf of the source of electrical energy

### EXAMPLE 4.3

مطابق معاشر تمارین

A heating element on an electric range operating on 240 V has a resistance of 30.0  $\Omega$ . What current does it draw?

Data:

(معادل)

$$E = 240 \text{ V}$$

$$R = 30.0 \Omega$$

$$I = ?$$

Basic Equation:

$$I = \frac{E}{R}$$

Working Equation: Same

Substitution:

$$I = \frac{240 \text{ V}}{30.0 \Omega}$$

$$= 8.0 \text{ V}/\Omega$$

$$= 8.0 \text{ A}$$

$$\boxed{\frac{V}{\Omega} = A}$$

$$\boxed{8.0 \text{ A}}$$

(ii)

# Electric Power

The rate of consuming energy is called power.

Unit = Watt (W)

$$P = V I$$

$P$  = power (watts)  
 $V$  = voltage drop (V)  
 $I$  = current (A)

$$\text{Thus, } 1 \text{ W} = 1 \text{ J/S}$$

Since the watt is a relatively small unit, the kilowatt ( $1 \text{ kW} = 1000 \text{ W}$ ) is commonly used in industry.

$$VA = \frac{J}{S} \cdot C = \frac{J}{S}$$

$$(V \cdot A) \rightarrow \frac{J}{S}$$

J/S

# Electric Power

Recalling Ohm's law,  $I = V/R$ , we find two other equations for power.

Given

$$I = \frac{V}{R}$$

substitute for  $V$  using  $V = IR$  to obtain

$$P = VI$$

$$P = (IR)I = I^2 R$$

$$P = I^2 R$$

Note from the following unit analysis that amps squared times ohms gives watts:

$$A^2 \Omega = A^2 \cdot \frac{V}{A} = AV = \frac{C}{s} \cdot \frac{J}{C} = \frac{J}{s} = W$$

$$I = \frac{V}{R} \Rightarrow P = I^2 R \Leftrightarrow P = \left(\frac{V}{R}\right)^2 R = \frac{V^2}{R^2} \cdot R \Leftrightarrow P = \frac{V^2}{R}$$

$$P = \frac{V^2}{R}$$

## EXAMPLE

A soldering iron draws 7.50 A in a 115-V circuit. What is its wattage rating?

Data:

$$I = 7.50 \text{ A}$$

$$V = 115 \text{ V}$$

$$P = ?$$

$$P = VI$$

$$P = V I$$

✓

Basic Equation:

Working Equation: Same

Substitution:

$$P = (115 \text{ V})(7.50 \text{ A})$$

$$= 863 \text{ W}$$

Therefore, a soldering iron drawing 7.50 A in a 115-V circuit has a rating of 863 W.

## EXAMPLE 4.5

A hand drill draws 4.00 A and has a resistance of 14.6  $\Omega$ . What power does it use?

Data:

$$I = 4.00 \text{ A}$$

$$R = 14.6 \Omega$$

$$P = ?$$

$$P = I^2 R$$

Basic Equation:

$$P = I^2 R$$

Working Equation: Same

Substitution:

$$P = (4.00 \text{ A})^2 (14.6 \Omega)$$

$$= 234 \text{ W}$$

Thus, a drill that draws 4.00 A with a resistance of 14.6  $\Omega$  has a rating of 234 W.

The amount of energy consumed is

$$\text{energy} = \frac{\text{power}}{\text{time}}$$

$$\text{energy} = \text{power} \times \text{time}$$

$$\text{energy} (\text{in kWh}) = (VI)t$$

$$\text{number of kWh} = Vit$$

$V$ (in Volts),  $I$ (in Amperes), and  $t$ (in seconds)

$$1 J = w \cdot t \cdot s$$

$$1 \text{ kWh} = 3.6 \times 10^9 \text{ J}$$

$$\frac{1 \text{ kWh}}{1000} = \frac{1}{3600}$$

Ques

$$E = P \cdot t$$

$P =$

$E =$

(K.W.H)

النفاذ

لـ ١٠٥٠ جرام

$$\text{cost} = P \times t \times \text{as well}$$

(kWh) (hours) (cents/kWh)

The cost of operating an electric device may be found as follows:

cost = energy  $\times$  cost per unit energy

Halala (h) in KSA

$$10^5 \text{ SAR}$$

kWh

price

$$\text{cost} = (\text{kWh}) \left( \frac{\text{cents}}{\text{kWh}} \right)$$

(kWh) (cents/kWh)

or

$$\text{cost} = P \times t \times \frac{1 \text{ kW}}{1000 \text{ W}} \times \frac{\text{cents}}{\text{kWh}}$$

price collection?

conversion factor  
Find the number of kWh.

$$t = \text{time in hours}$$

$$P = \text{power in kW}$$

$$(4) \text{ multiply } (\text{kWh}) \text{ by the price } (\text{SAR}/\text{kWh})$$

نادي اسمنت الراشدية المكرر بالشيف

نادي اسمنت الراشدية  
نادي اسمنت الراشدية

Saudi Electricity Company  
نادي اسمنت الراشدية

١٤٣١/١١/١٥  
١٤٣١/١١/١٦  
١٤٣١/١١/١٧  
٩٢٠٠١١٠٠

٩٣٣  
٩٣٣  
٩٣٣  
٩٣٣

نادي اسمنت الراشدية  
نادي اسمنت الراشدية  
نادي اسمنت الراشدية  
نادي اسمنت الراشدية

١٤٣١/١١/١٨  
١٤٣١/١١/١٩  
١٤٣١/١١/٢٠  
١٤٣١/١١/٢١

٩٣٣  
٩٣٣  
٩٣٣  
٩٣٣

بيان مصادر

١٤٣١/١١/٢٢  
١٤٣١/١١/٢٣  
١٤٣١/١١/٢٤  
١٤٣١/١١/٢٥

٩٣٣  
٩٣٣  
٩٣٣  
٩٣٣

| بيان المصادر | بيان المصادر | بيان المصادر | بيان المصادر |
|--------------|--------------|--------------|--------------|
| ١٤٣١/١١/٢٢   | ١٤٣١/١١/٢٣   | ١٤٣١/١١/٢٤   | ١٤٣١/١١/٢٥   |
| ٩٣٣          | ٩٣٣          | ٩٣٣          | ٩٣٣          |
| ٩٣٣          | ٩٣٣          | ٩٣٣          | ٩٣٣          |
| ٩٣٣          | ٩٣٣          | ٩٣٣          | ٩٣٣          |

| بيان المصادر | بيان المصادر | بيان المصادر | بيان المصادر |
|--------------|--------------|--------------|--------------|
| ١٤٣١/١١/٢٢   | ١٤٣١/١١/٢٣   | ١٤٣١/١١/٢٤   | ١٤٣١/١١/٢٥   |
| ٩٣٣          | ٩٣٣          | ٩٣٣          | ٩٣٣          |
| ٩٣٣          | ٩٣٣          | ٩٣٣          | ٩٣٣          |
| ٩٣٣          | ٩٣٣          | ٩٣٣          | ٩٣٣          |

| بيان المصادر | بيان المصادر | بيان المصادر | بيان المصادر |
|--------------|--------------|--------------|--------------|
| ١٤٣١/١١/٢٢   | ١٤٣١/١١/٢٣   | ١٤٣١/١١/٢٤   | ١٤٣١/١١/٢٥   |
| ٩٣٣          | ٩٣٣          | ٩٣٣          | ٩٣٣          |
| ٩٣٣          | ٩٣٣          | ٩٣٣          | ٩٣٣          |
| ٩٣٣          | ٩٣٣          | ٩٣٣          | ٩٣٣          |

|            |            |            |            |
|------------|------------|------------|------------|
| ١٤٣١/١١/٢٢ | ١٤٣١/١١/٢٣ | ١٤٣١/١١/٢٤ | ١٤٣١/١١/٢٥ |
| ٩٣٣        | ٩٣٣        | ٩٣٣        | ٩٣٣        |
| ٩٣٣        | ٩٣٣        | ٩٣٣        | ٩٣٣        |
| ٩٣٣        | ٩٣٣        | ٩٣٣        | ٩٣٣        |
| ٩٣٣        | ٩٣٣        | ٩٣٣        | ٩٣٣        |

Example:

$$1500 \text{ kWh} \rightarrow 1500 \text{ kWh} \times$$

$$5h = 75 \text{ RS}$$

| بيان المصادر | بيان المصادر | بيان المصادر | بيان المصادر |
|--------------|--------------|--------------|--------------|
| ١٤٣١/١١/٢٢   | ١٤٣١/١١/٢٣   | ١٤٣١/١١/٢٤   | ١٤٣١/١١/٢٥   |
| ٩٣٣          | ٩٣٣          | ٩٣٣          | ٩٣٣          |
| ٩٣٣          | ٩٣٣          | ٩٣٣          | ٩٣٣          |
| ٩٣٣          | ٩٣٣          | ٩٣٣          | ٩٣٣          |
| ٩٣٣          | ٩٣٣          | ٩٣٣          | ٩٣٣          |

An iron is rated at 550 W. How much would it cost to operate it for 2.50 h at \$0.08/kWh?

**Data:**

$$P = 550 \text{ W}$$

$$t = 2.50 \text{ h}$$

$$R = 0.08 \text{ \$/kWh}$$

$$\text{rate} = \$0.08/\text{kWh}$$

$$\text{cost} = ?$$

$$\begin{aligned} C &=? \\ t &= 2.5 \text{ h} \\ R &= 0.08 \text{ \$/kWh} \\ \Rightarrow C &= P \times t \times \frac{\$}{\text{kWh}} \\ &= 550 \times 2.5 \times \frac{0.08 \text{ \$}}{\text{kWh}} \\ &= 0.11 \text{ \$.} \end{aligned}$$

**Basic Equation:**

$$\text{cost} = P \times \left( \frac{1 \text{ kWh}}{1000 \text{ W}} \right) \left( \frac{\text{cents}}{\text{kWh}} \right)$$

**Working Equation:** Same

**Substitution:**

$$\begin{aligned} \text{cost} &= (550 \text{ W}) (2.50 \text{ h}) \left( \frac{1 \text{ kWh}}{1000 \text{ W}} \right) \left( \frac{\$0.08}{\text{kWh}} \right) \\ &= \$0.11 \end{aligned}$$



# Electric Circuits

الدوائر الكهربائية

الكلمة

Source مصادر الطاقة

Symbol رسم

Circuit with a bulb  
and a switch


(Figure 1)

Light bulb

Switch

Load

Source

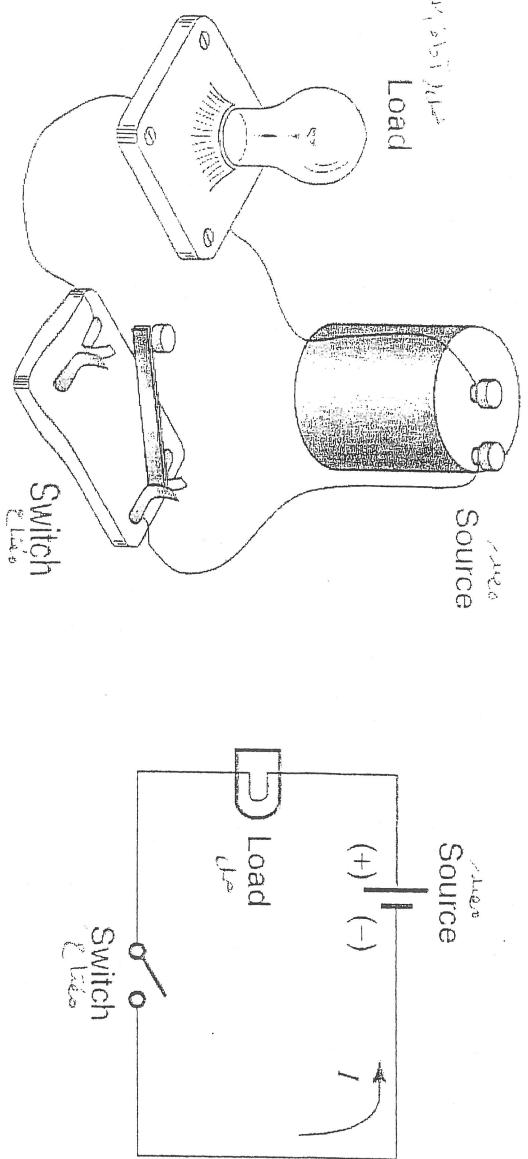

Picture diagram

(a)

Symbol diagram

(b)

represents the resistance (load)  
— represents the switch

represents the source (the short line represents the negative terminal and the long line represents the positive terminal)

Circuit diagram

(c)


# SERIES CIRCUITS

المواء

دواء

SERIES توازي

$I = I_1 = I_2 = I_3 = \dots$

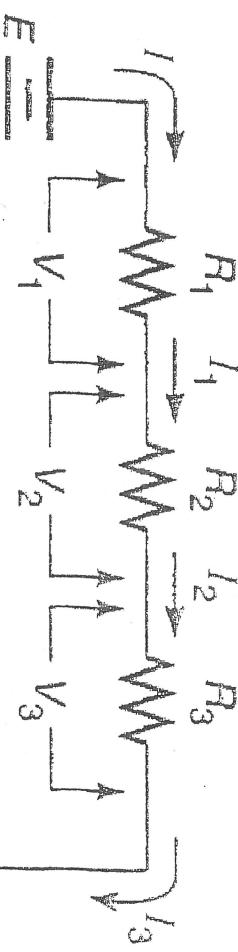

$I = \frac{\text{total voltage}}{\text{total resistance}}$   $I_1 = \text{current through } R_1$   
 $I_2 = \text{current through } R_2$   $I_3 = \text{current through } R_3$

## SERIES

$E = V_1 + V_2 + V_3 + \dots$

$V_s$  = emf of the source  $V_1$  = voltage drop across  $R_1$

$V_2$  = voltage drop across  $R_2$   $V_3$  = voltage drop across  $R_3$

An electric circuit with only one path for the current to flow is called a **series circuit**.

مهمة ملحوظة: هناك سبعة مفاهيم متعلقة بالمواء

$R = R_1 + R_2 + R_3 + \dots$

$R$  = total or equivalent resistance of the circuit  $R_1$  = resistance of first load

$R_2$  = resistance of second load  $R_3$  = resistance of third load

$$R = R_1 + R_2 + R_3 + \dots \quad (1)$$

$$E = V_1 + V_2 + \dots \quad (2)$$

$$I = I_1 = I_2 = I_3 = \dots \quad (3)$$



## EXAMPLE 4.7

Find the total resistance of the circuit shown in Figure 4.8.

Data:

$$R_1 = 7.00 \Omega$$

$$R_2 = 9.00 \Omega$$

$$R_3 = 21.0 \Omega$$

$$R = ?$$

Basic Equation:

$$R = R_1 + R_2 + R_3$$

Working Equation: Same

Substitution:

$$\begin{aligned} R &= 7.00 \Omega + 9.00 \Omega + 21.0 \Omega \\ &= 37.0 \Omega \end{aligned}$$

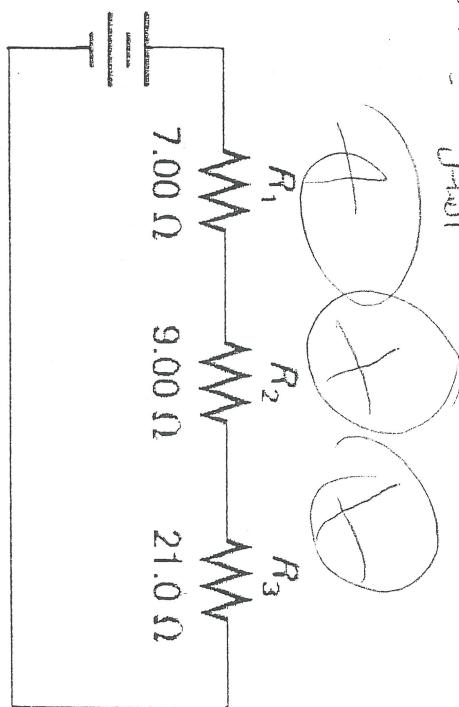


FIGURE 4.8

## EXAMPLE 4.8

Find the current in the circuit shown in Figure 4.9.

**Data:**

$$R_1 = 5.00 \Omega \quad R_4 = 96.0 \Omega$$

$$R_2 = 13.0 \Omega \quad E = 90.0 \text{ V}$$

$$R_3 = 12.0 \Omega \quad I = ?$$

**Basic Equations:**  $R = R_1 + R_2 + R_3 + R_4$  and  $I = \frac{E}{R}$

**Working Equations:** Same


**Substitutions:**

$$R = 5.00 \Omega + 13.0 \Omega + 12.0 \Omega + 96.0 \Omega$$

$$= 126.0 \Omega$$

$$I = \frac{90.0 \text{ V}}{126.0 \Omega}$$

$$= 0.714 \text{ A}$$

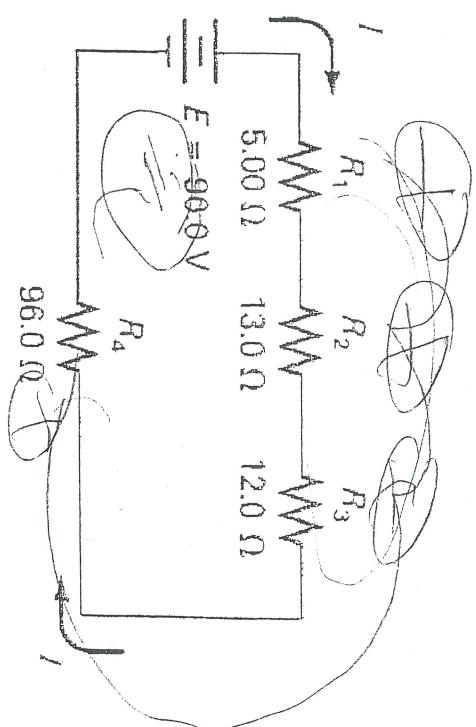

**FIGURE 4.9**

## EXAMPLE 4.9


Find the value of  $R_3$  in the circuit shown in Figure 4.10.

**Data:**

$$I = 3.00 \text{ A} \quad R_2 = 14.0 \Omega$$

$$E = 115 \text{ V} \quad R_3 = ?$$

$$R_1 = 23.0 \Omega$$

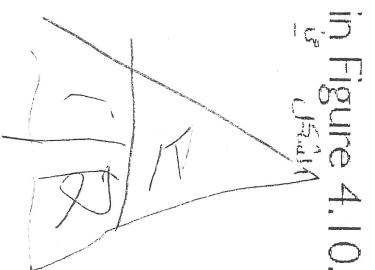

**Basic Equations:**  $I = \frac{E}{R}$  and  $R = R_1 + R_2 + R_3$

**Working Equations:**

$$R = \frac{E}{I} \quad \text{and} \quad R_3 = R - R_1 - R_2$$

**Substitutions:**

$$R = \frac{E}{I} \quad \text{and} \quad R_3 = R - R_1 - R_2$$

$$R = \frac{E}{I} = \frac{115 \text{ V}}{3.00 \text{ A}} = 38.3 \Omega$$

$$R_3 = 38.3 \Omega - 23.0 \Omega - 14.0 \Omega$$

$$= 1.3 \Omega$$

**FIGURE 4.10**

$$R = R_1 + R_2 + R_3$$

$$R = 23 + 14 + R_3$$

(R)  $\leftarrow$

$$\frac{I}{E} = \frac{R}{R} \Rightarrow E = I \cdot R$$

$$R = \frac{E}{I} = \frac{115}{3} = 38.3 \Omega$$

$$38.3 = 23 + 14 + R_3$$

$$38.3 - 23 - 14 = R_3$$

$$R = R_1 + R_2 + R_3$$

$$R = 23 + 14 + R_3$$

$$38.3 = 23 + 14 + R_3$$

## EXAMPLE 4.10

Find the voltage drop across  $R_3$  in Figure 4.10.


Data:

$$I = I_3 = 3.00 \text{ A}$$

$$R_3 = 1.3 \Omega$$

$$V_3 = ?$$

$$1.3 \Omega$$

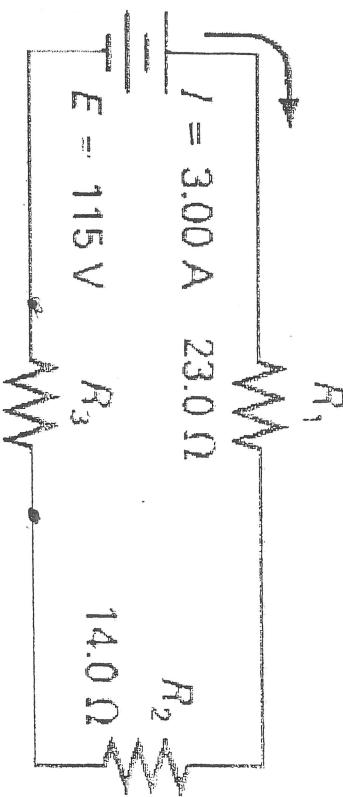

Basic Equation:

$$I_3 = \frac{V_3}{R_3}$$

$$\begin{aligned} I &= \frac{V}{R} \\ V &= I \cdot R \end{aligned}$$

FIGURE 4.10

Working Equation:

$$V_3 = I_3 R_3$$


Substitution:

$$\begin{aligned} V_3 &= (3.00 \text{ A})(1.3 \Omega) \\ &= 3.9 \text{ V} \end{aligned}$$



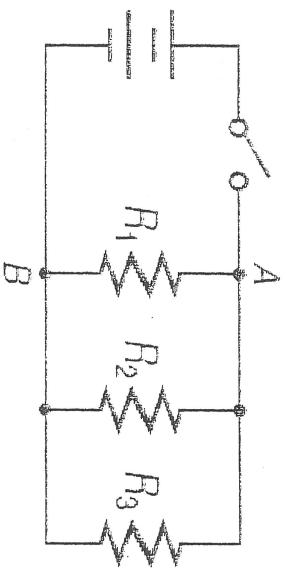
# PARALLEL CIRCUITS

An electric circuit with more than one path for the current to flow is called a parallel circuit.

Different ways to represent a parallel circuit



Or

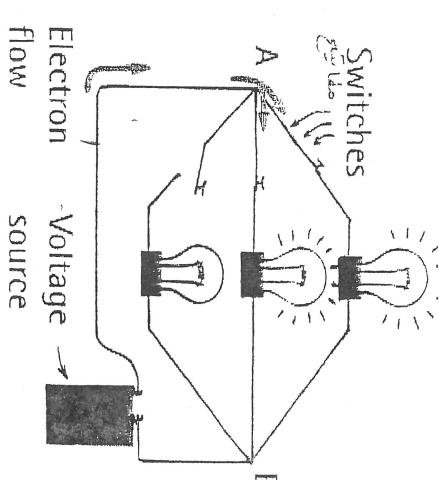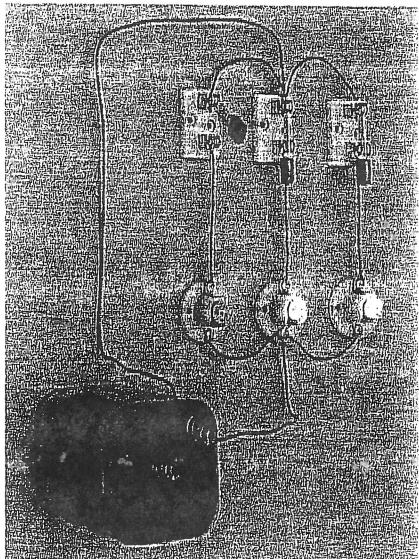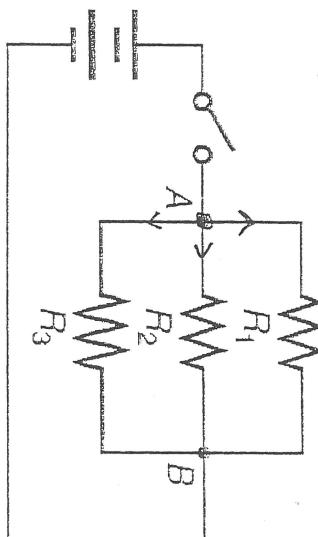

$$E = V_1 + V_2 + V_3 + \dots \quad (1)$$

$$I = I_1 + I_2 + I_3 + \dots \quad (2)$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \quad (3)$$

Electron flow  
نذریکرنا

(2)

# PARALLEL CIRCUITS

*J. H. S.*

*circuit parallel*


$$I = I_1 + I_2 + I_3 + \dots$$

*I = total current in the circuit*

*I<sub>1</sub> = current through R<sub>1</sub>*

*I<sub>2</sub> = current through R<sub>2</sub>*

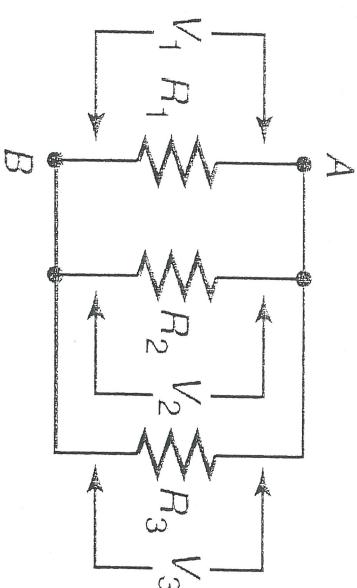*I<sub>3</sub> = current through R<sub>3</sub>*



$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

*R = equivalent resistance*

*R<sub>1</sub> = resistance of R<sub>1</sub>*

*R<sub>2</sub> = resistance of R<sub>2</sub>*

*R<sub>3</sub> = resistance of R<sub>3</sub>*

*circuit parallel*

$$V_1 = V_2 = V_3 = \dots$$

$$E = V_1 = V_2 = V_3.$$

*circuit parallel with voltage source*

$$E = V_1 = V_2 = V_3 = \dots$$


$$E = V_1 = V_2 = V_3.$$

*E = emf of the source*


*V<sub>1</sub> = voltage drop across R<sub>1</sub>*

*V<sub>2</sub> = voltage drop across R<sub>2</sub>*

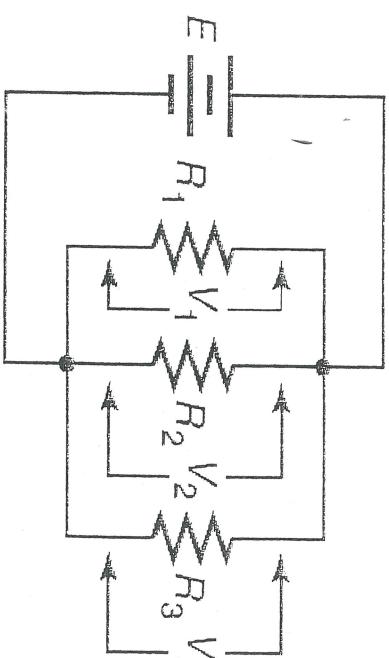*V<sub>3</sub> = voltage drop across R<sub>3</sub>*




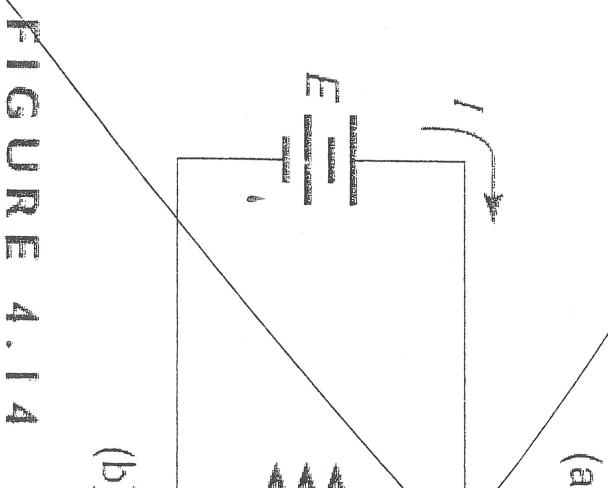If the parallel combination of resistances is replaced by a single resistance with the resistance  $R$ , the same current flows in the circuit.



$$R = \frac{R_1 R_2}{R_1 + R_2}$$

(b)


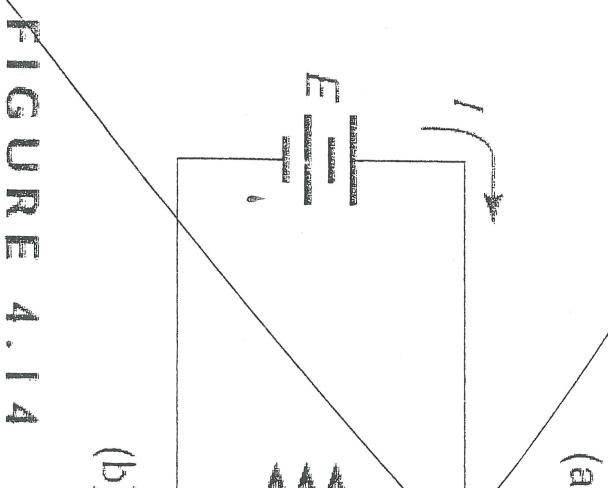


(b)

FIGURE 4.14

Resistor  $R$  in part (b) is equivalent to the pair of resistances  $R_1$  and  $R_2$  connected in parallel in part (a).

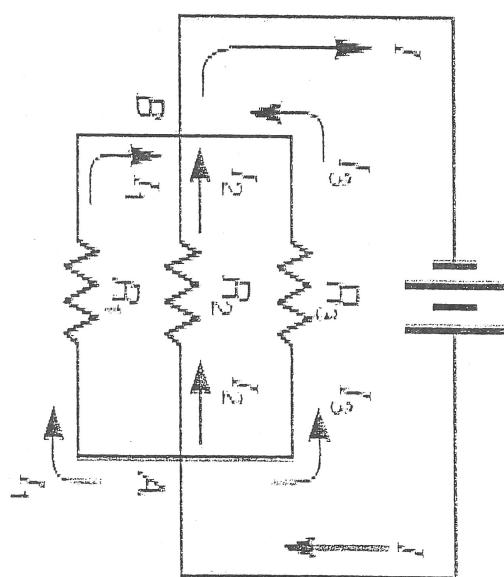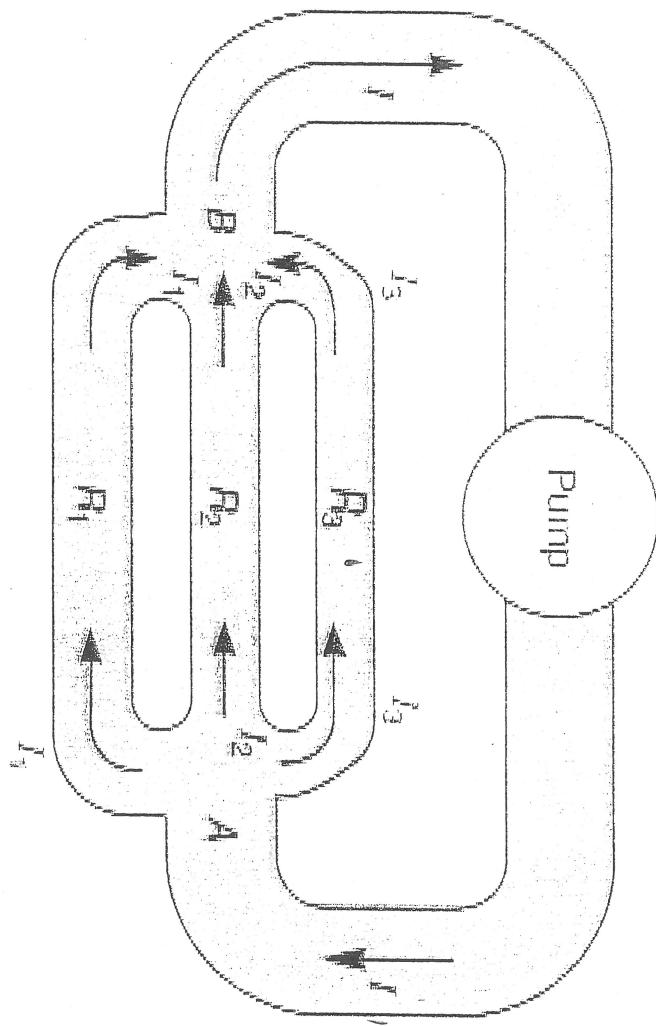A water system may be compared to a parallel electric circuit.



(3)

## EXAMPLE 4.11

Find the equivalent resistance of the circuit shown in Figure 4.16.

Data:

$$R_1 = 7.00 \Omega$$

$$R_2 = 9.00 \Omega$$

$$R_3 = 12.0 \Omega$$

$$R = ?$$

Basic Equations:

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Working Equation:

When using this formula, you should solve for the reciprocal of the unknown, then substitute.

Substitution:

$$\frac{1}{R} = \frac{1}{7.00 \Omega} + \frac{1}{9.00 \Omega} + \frac{1}{12.0 \Omega}$$

$$R = 2.96 \Omega$$

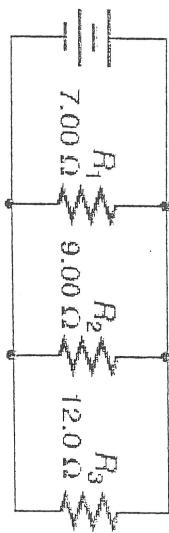


FIGURE 4.16

$$\frac{1}{R} = \frac{1}{7} + \frac{1}{9} + \frac{1}{12}$$

$$\frac{1}{R} = \frac{85}{252}$$

$$R = \frac{252}{85}$$

$$R = 2.964$$

معلمات

(2)

## EXAMPLE

Find the total current in the circuit shown in Figure 4.17.

**Data:**

$$R_1 = 23.0 \Omega$$

$$R_2 = 14.0 \Omega$$

$$R_3 = 5.00 \Omega$$

$$E = 90.0 \text{ V}$$

$$I = ?$$

First, find the equivalent resistance,  $R$ . Second, find the total current,  $I$ . To find  $R$ :

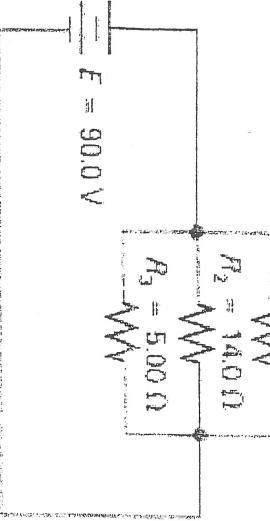


FIGURE 4.17

**Basic Equation:**

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

**Working Equation:** Same

**Substitution:**

$$\frac{1}{R} = \frac{1}{23.0 \Omega} + \frac{1}{14.0 \Omega} + \frac{1}{5.00 \Omega}$$

Using a calculator sequence as in Example 4.11, we find

$$R = 3.18 \Omega$$

To find  $I$ :

**Basic Equation:**

$$I = \frac{E}{R}$$

**Working Equation:** Same

**Substitution:**

$$I = \frac{90.0 \text{ V}}{3.18 \Omega}$$

$$= 28.3 \text{ A}$$

### EXAMPLE 4.13

Find the current through  $R_2$  in Figure 4.17 from Example 4.12.

Data:

$$R_2 = 14.0 \Omega$$

$$E = 90.0 V = V_2$$

$$I_2 = ?$$

Basic Equation:

$$I_2 = \frac{V_2}{R_2}$$

Working Equation: Same

Substitution:


$$I_2 = \frac{90.0 V}{14.0 \Omega}$$

$$= 6.43 A$$

$$I_2 = \frac{V}{R_2}$$

$$= \frac{90}{14}$$

$$= 6.43$$

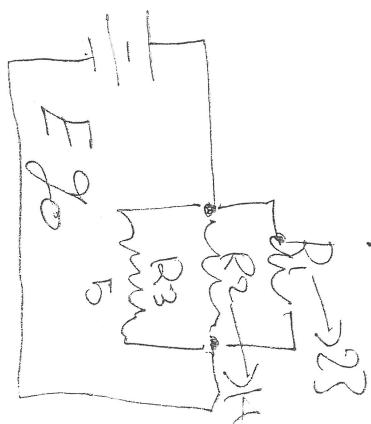

## EXAMPLE 4.14

Find the equivalent resistance and the value of  $R_3$  in the circuit shown in Figure 4.18.

Data:

$$E = 115 \text{ V}$$

$$I = 7.00 \text{ A}$$


$$R_1 = 38.0 \Omega$$

$$R_2 = 49.0 \Omega$$

$$R_3 = ?$$

*Wing*

Substitution:

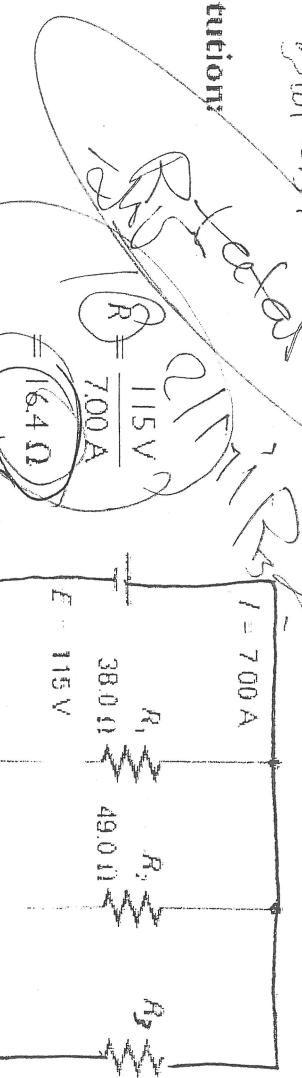

To find  $R_3$ :

Basic Equation:

First find  $R$ :

Basic Equation:

Working Equation:

$$I = \frac{E}{R}$$

Working Equation:

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_3} = \frac{1}{R} - \frac{1}{R_1} - \frac{1}{R_2}$$

Working Equation:

$$R = \frac{E}{I}$$

Substitution:

$$\frac{1}{R_3} = \frac{1}{115} - \frac{1}{38.0} - \frac{1}{49.0}$$

~~$R_3 = 16.4 \Omega$~~

$$= 16.4 \Omega$$

$$R_3 = \frac{115}{7.00} = 16.4 \Omega$$

FIGURE 4.18