



EE 212 - ELECTRONICS I

Fall semester 2017

QUIZ 3

Grade

10

Name, Family Name: _____

ID No.: _____ Section No.: 1050 Signature: _____

Quiz Duration: 15 minutes.

Instructions: Write "the correct" answer in the space provided under each question.

Question: [CO_7, PI_5_53, SO_5]


Calculate the following parameter for Common Emitter Bias configuration

Z_i

Z_o

A_v

to calculate Z_i we need R_{re}

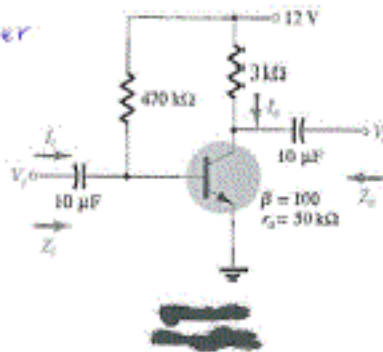

Solution:

we need R_{re}

$$I_B = \frac{12 - 0.7}{470k} = 24.04 \mu A$$

$$I_E = (\beta + 1) I_B \Rightarrow (101)(24.04 \mu A) = 2.43 mA$$

$$r_e = \frac{26 mV}{(101)(24.04 \mu A)} = 10.708 \Omega$$

$$Z_i = R_B \parallel R_{re} \Rightarrow \frac{470k \times 10.708 \times 100}{470k + 10.708 \times 100}$$

$$= 1069.25 \Omega$$

$$Z_o = \frac{3k \times 50k}{3k + 50k} = 2830.19 \Omega$$

$$A_v = \frac{-R_c}{r_e} = \frac{-3k}{10.708}$$

$$= -280.16 V$$

2830.18



EE 212 - ELECTRONICS I

Fall Semester 2017

QUIZ 2

Grade
(7)

Name, Family Name: [Redacted]

ID No.: [Redacted] Section No.: 1050 Signature: [Redacted]


Quiz Duration: 15 minutes.

Instructions: Write "the correct" answer in the space provided under each question.

Question: [CO_5, PI_5_49, SO_5]

Q1. Figure below shows typical characteristic curve for BJT transistor. For maximum power value calculate V_{CE} and I_C at least on 2 point. Show those points on the curves. (8)

Q2. What value BV_{CEO} Represent? (2)

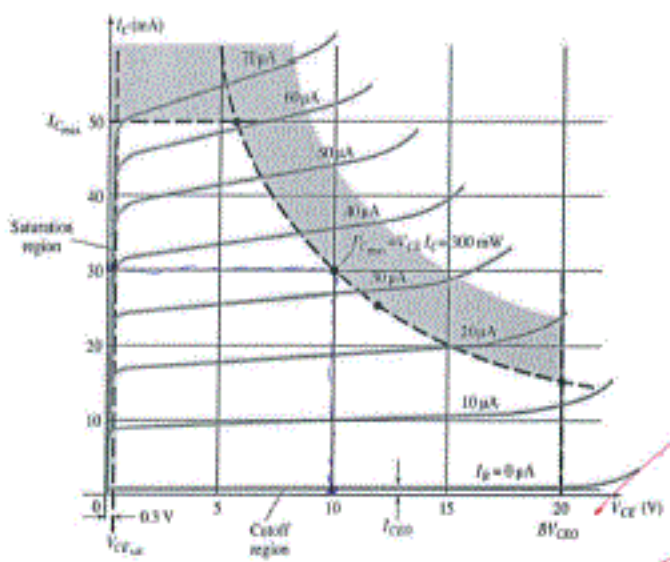

$$P_{CE} = I_C V_{CE}$$

$$V_{CE} = \frac{P}{I}$$

Ans. 1) $I_C = 30 \text{ mA}$

$V_{CE} = 10 \text{ V}$

Second point

Ans. 2) It represents the Break down voltage b/w emitter and collector.



EE 212 - ELECTRONICS I

Fall 2017

QUIZ 1

Grade

2

Name, Family Name : _____

ID No.: _____ Section No.: 2888 Signature: _____


Quiz Duration: 15 minutes.

Instructions: Write "the correct" answer in the space provided under each question.

Question: [CO_3, PI_5_51, SO_5]

Consider the diode circuit shown in Figure P1.

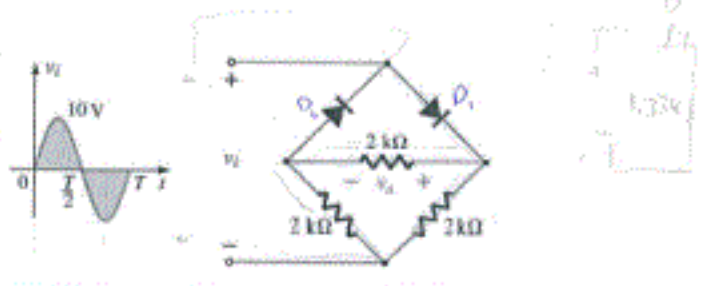- (a) Draw the output wave form (10 points)
(b) Calculate the output DC level. (10 points)
(c) Calculate the PIV for each diode (5 points)



Solution:

a) $I = \frac{V_o}{R} = \frac{1.334}{2k} = 0.667 \text{ mA}$

$I_o = \frac{2k}{6k} \times 0.667 \times 10^{-3} = 0.222 \text{ mA}$


$\Rightarrow V_o = (0.222 \text{ mA})(2k) = 0.444 \text{ V}$

b) $V_{dc} = 0.318 V_p \Rightarrow V_{dc} = (0.318)(1.334) = 0.424 \text{ V}$
for half cycle

for full to $0.638(V_p)$

c) for D_1 PIV $< -10 \text{ V}$ like if it's -10 V it'll breakdown

for D_2 PIV $> 10 \text{ V}$ like if it's 10 V

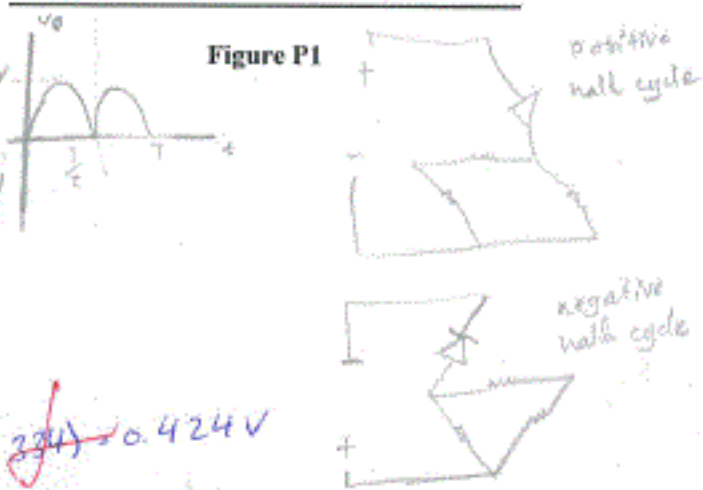



EE 212 - ELECTRONICS I

Fall Semester 2017

QUIZ 4

Grade

7

Name, Family Name: _____

ID No.: _____ Section No.: 1050 Signature: _____



Quiz Duration: 15 minutes.

Instructions: Write "the correct" answer in the space provided under each question.

Question: [CO_9, PI_1_73, SO_1]

[CO_4, PI_5-54, SO_5]

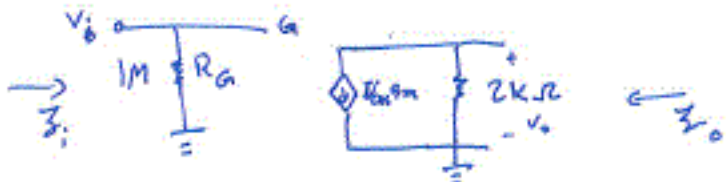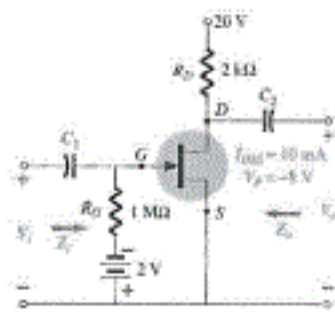Question 1. Calculate the Input impedance, Output Impedance and Voltage gain for JFET Amplifier



$Z_i = R_G = 1 M\Omega$ ✓

$Z_o = R_D = 2 k\Omega$ ✓

$A_v = -g_m R_D$

$g_m = g_{m0} \left(1 - \frac{V_P}{V_{GS}}\right)$

$V_{GS} = -V_{GS} = -2V$

$g_{m0} = \frac{2 I_{DSS}}{|V_P|} = \frac{(2)(10mA)}{8} = 2.5 mA/V$ ✓

$g_m = 2.5m \left(1 - \frac{V_P}{V_{GS}}\right) \Rightarrow 2.5m \left(1 - \frac{-8}{-2}\right) = -7.5 mA/V$

~~$g_m = \frac{2 I_{DSS}}{|V_P|} \left(1 - \frac{V_P}{V_{GS}}\right)$~~

$A_v = -(-7.5m)(2k) = 15$