



EE 202 – CIRCUIT THEORY II

Fall Semester 2017-2018

Midterm Exam 1

Exam Date: November 06, 2017; Exam Duration: 90 minutes

Student's Full Name: _____

Student ID #: _____ Section #: 1053 Signature: _____

Instructions:

- Write your student ID number on the top of each page
- Write the solution in the space provided under each question
- Show all the details of your analysis and calculations

Question No.	Points Assigned	Points Awarded
1. [CO_6, PI_11_14, SO_11]	34	31
2. [CO_2, PI_1_27, SO_1]	33	19
3. [CO_5, PI_11_14, SO_11]	33	13
Total	100	53

Question 3 - (solution Continued)

Unit step: it's internal when we closed the ~~circuit~~ circuit
at the unit step mean it's very small drop internal
when we close the circuit to get the same value for
(sources voltage or current) like




impulses functions : this function it's get the same value
when we close the ~~circuit~~ circuit (so no unit step)

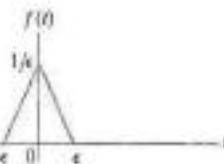Question 3

Find the Laplace transform of (show steps)

- The derivative of unit step function (9 points) = 1
- $\cos \omega t$ (9 points)
- What is the magnitude of $f(0)$ when $c=0$? (7 points)
- What is unit step and impulse functions? (8 points)



$$\frac{d}{ds} F(s) = 1$$

Solution

~~$$F(s) = \int F(s) ds$$~~


~~$$\int F(s) ds$$~~



$$\frac{d}{ds} F(s) = 1$$

$$\left. \frac{d}{ds} F(s) \right|_{s=0} = 0 \quad \Rightarrow \quad 1 - 0 = 1$$

$$\frac{d}{ds} F(s) = 0$$

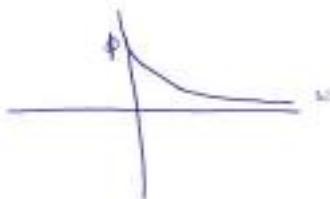

b) $\cos \omega t = \frac{1}{(s+a)^2 + \omega^2}$



c) $f(0) = \frac{1}{\omega} = \infty$



b) $P = |s| \cos \theta$

$Q = |s| \sin \theta$

$$P = iV = ((49, 906 + 3, 7479) \times 3) \\ = 449,718 + 11,241i$$


c) $R_L = \sqrt{R_{in}^2 + (X_L + X_m)^2}$

d) $P = \frac{1}{n} \frac{V}{R}$

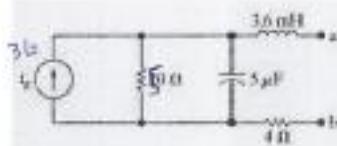Question 2

The source current in the circuit shown is $3 \cos 100t$ A as shown in figure, when value of resistor is taken 50 ohm instead of 20 ohm.

- What impedance should be connected across terminals a, b for maximum average power transfer? 8 points
- What is the average power transferred to the impedance in (a)? 9 points
- Assume that the load is restricted to pure resistance. What size resistor connected across a,b will result in the maximum average power transferred? 9 points
- What is the average power transferred to the resistor in (c)? 7 points



Solution

$$Z_L = Z_{Th}$$


$$V = 3 \times 50 = 150 \text{ V}$$

$$w = 100 \Rightarrow X_L = wL = 0.36 \Omega \quad \left\{ X_C = \frac{1}{wC} = 2000 \Omega \right.$$

$$V_{Th} = \frac{150}{20 + j50} \cdot 150 = 149.906 + 3.747j$$

$$\text{so } Z_{Th} = \frac{V_{Th}}{I} = \frac{149.906 + 3.747j}{3} = 49.968 + 1.24j$$

$$\Rightarrow Z_L = 49.968 - 1.24j$$

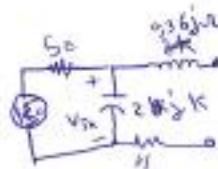

phasor
eq?

Thévenin
eq.

$$\text{so } k_3 = k_1 \Rightarrow k_3 = -15$$

$$\text{And } k_4 = k_2 \Rightarrow k_4 = -15i$$

~~29~~ 29

$$\Rightarrow \frac{60}{(s^2+4s+5)^2} = \frac{-15}{(s+2+i)^2} + \frac{15i}{(s+2+i)} + \frac{-15}{(s+2-i)^2} + \frac{-15i}{(s+2-i)}$$

so Laplace invers

$$\underline{L}(f(s)) = -15 + e^{-(s+2)+i} + 15i e^{-(s+2)+i} - 15 + e^{-(s+2)-i} - 15i e^{-(s+2)-i}$$

~~Poles: it's limit of f(s) when s → ∞~~

~~$\lim_{s \rightarrow \infty} f(s)$~~

2

~~Zeros: it's limit of f(s) when s → 0~~

~~$\lim_{s \rightarrow 0} f(s)$~~