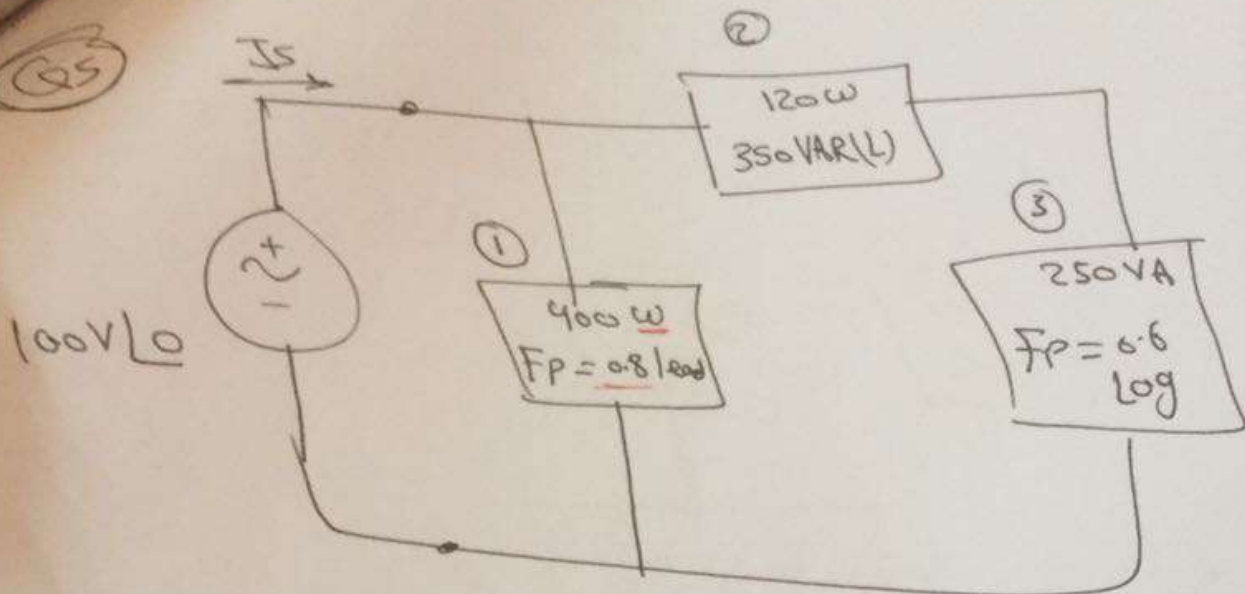


Q5



Find P_T & Q_T & S_T & FP & I_s & Z_{in} & X_c

Solution

①

$$P_1 = 400 \text{ W}$$


$$FP = 0.8 \text{ (lead)}$$

$$\theta = \cos^{-1} 0.8 = 36.87$$

$$Q_1 = P_1 \tan \theta = 400 \tan 36.87 =$$

$$Q_1 = -300 \text{ VAR}$$

↓
lead.

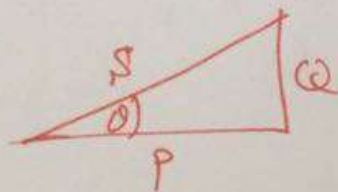

line current

$$I_{\text{line}} = \sqrt{3} I_{\text{ph}} \angle -30$$

$$I_{Aa} = \sqrt{3} \times 8 \angle -36.87$$

←
2.5WV

$$I_{Aa} = 8\sqrt{3} \angle -66.87 \text{ A}$$

$$I_{Bb} = I_{Aa} \angle -120 = 8\sqrt{3} \angle -66.87 - 120$$


$$I_{Cc} = I_{Aa} \angle +120 = 8\sqrt{3} \angle -66.87 + 120$$

V_R ??

$$V_R = I_{ab} \times R$$

$$V_R = 20 \times 8 \angle -36.87$$

$$V_R = 160 \angle -36.87 \checkmark$$

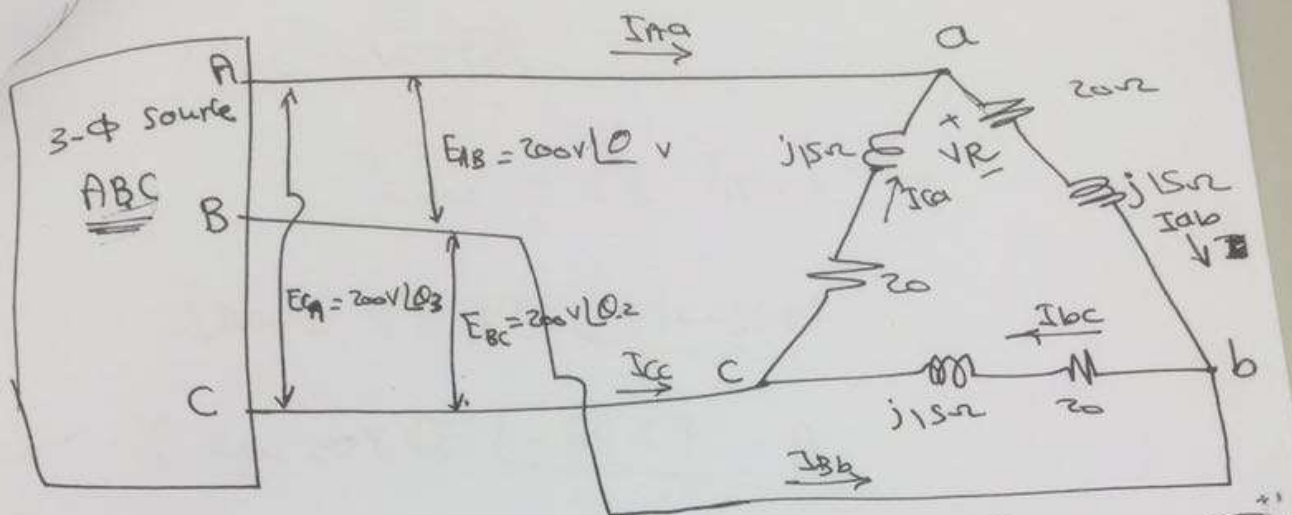

a) find ϕ_2 & ϕ_3 .

$$\phi_2 = -120^\circ$$

$$\phi_3 = +120^\circ$$

AB	→	0
ϕ_2 → BC	→	-120
ϕ_3 → CA	→	+120

b) I_{ab}, I_{bc}, I_{ca}

$$V_{ab} = E_{ab} = 200 \angle 0^\circ \text{ V}$$

$$I_{ab} = \frac{V_{ab}}{Z_{ab}} = \frac{200 \angle 0^\circ}{20 + j15} = 8 \angle -36.87^\circ$$

(ABC) +ve

$$I_{bc} = I_{ab} \angle -120^\circ = 8 \angle -36.87^\circ - 120^\circ$$

$$I_{ca} = I_{ab} \angle +120^\circ = 8 \angle -36.87^\circ + 120^\circ$$

$$I_{ca} = -I_{ac}$$

$$F_P = \left(\frac{|P_T|}{|S_T|} \right) = \frac{670}{715.12} = 0.936 \text{ Log}$$

\leftarrow $\frac{|P_T|}{|S_T|}$ \leftarrow $\frac{670}{715.12}$ \leftarrow 0.936 Log

$$S = V_s I_s^*$$

$$I_s^* = \frac{S}{V_s} = \frac{715.12 \angle 20.46}{100 \angle 0}$$

$$I_s^* = 7.15 \angle 20.46$$

$$I_s = 7.15 \angle -20.46 \text{ A}$$

$$Z_{in} = \frac{V_s}{I_s} = \frac{100 \angle 0}{7.15 \angle -20.46}$$

$$Z_{in} = 13.98 \angle 20.46 \Omega$$

2)

$$P_2 = 120 \text{ W}$$

$$Q_2 = +350 \text{ VAR}$$


مقاومة
مكثف

3)

$$S_3 = 250 \text{ VA}$$

$$F_p = 0.6 \text{ Lag}$$

$$\theta = \cos^{-1} 0.6 = 53.13^\circ$$

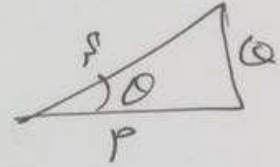

$$P_3 = S \cos \theta = 250 \times \cos 53.13^\circ = 150 \text{ W}$$

$$Q_3 = S \sin \theta = 250 \times \sin 53.13^\circ = +200 \text{ VAR}$$

Lag ←

$$P_T = P_1 + P_2 + P_3$$

$$= 400 + 120 + 150 = 670 \text{ W}$$


$$Q_T = Q_1 + Q_2 + Q_3$$

$$= -300 + 350 + 200 = +250 \text{ VAR}$$

$$S_T = P_T + jQ_T = 670 + j250 \text{ VA}$$

$$S_T = 715.12 \angle 20.46^\circ \text{ VA}$$

Q5

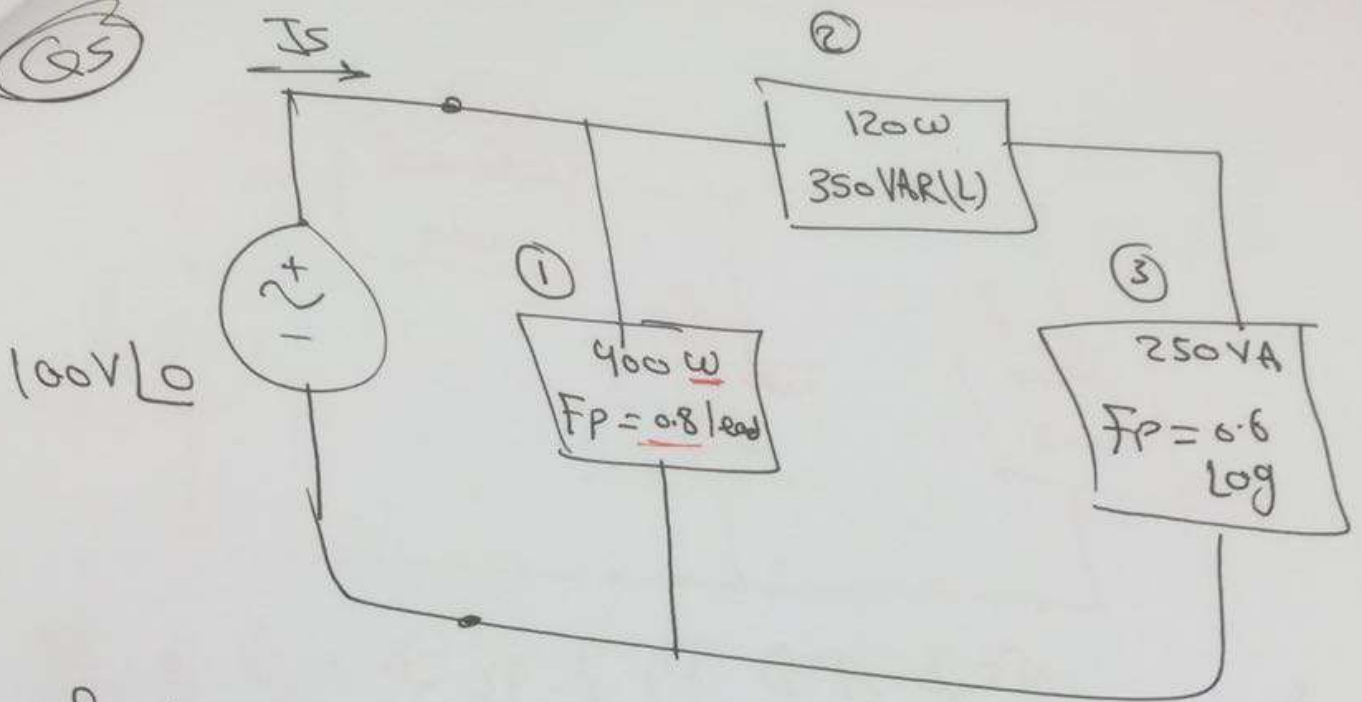

Find P_T & Q_T & S_T & FP & I_S & Z_{in} & X_c

Solution

①

$$P_1 = 400 \text{ W}$$

$$\text{FP} = 0.8 \text{ (lead)}$$


$$\theta = \cos^{-1} 0.8 = 36.87^\circ$$

$$Q_1 = P_1 \tan \theta =$$

$$= 400 \tan 36.87 =$$

$$Q_1 = -300 \text{ VAR}$$

lead.

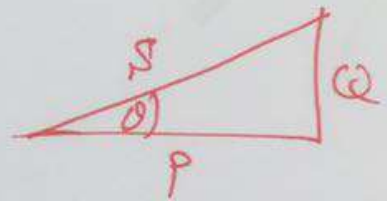

$$\underline{S_{load}} = 3 V_{ph} I_{ph}^*$$

$$= 3 V_{ab} I_{ab}^*$$

$$S_{load} = 3 (200 \angle 0) (8 \angle +36.87)$$

$$S_{load} = 3840 \text{ (P)} + j2880 \text{ (Q) VA}$$

$$S_{load} = 4800 \angle 36.87 \text{ VA}$$

$$F.P. = \frac{(P_T)}{(S_T)} = \frac{3840}{4800}$$

$$F.P. = 0.8 \text{ Lag}$$

~~M.P.~~ Q_T \swarrow