
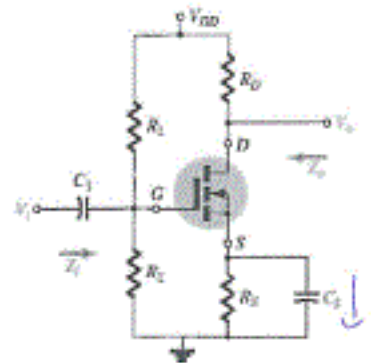


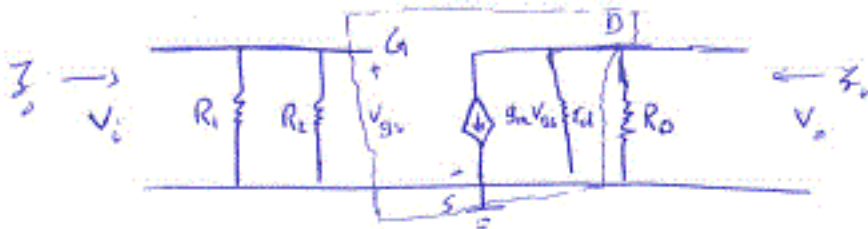
**Question 6 (10 points)**

- Draw the small signal model of E-MOSFET
- Derive the relationship for Input/output Impedance and Voltage gain.



$$Z_i = R_1 \parallel R_2$$

$$Z_o = R_D \parallel r_d$$

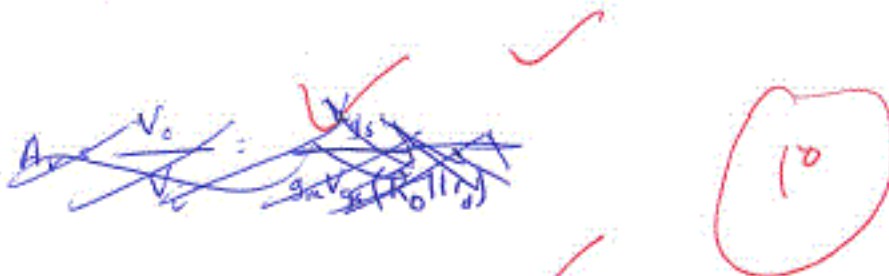

$$A_v = \frac{V_o}{V_i} = \frac{-g_m V_{gs} (R_D \parallel r_d)}{V_{gs}} = -g_m (R_D \parallel r_d)$$

**Question 5 (10 points)**

(a) For the given JFET the  $V_s$  is 1.7V, Find

$I_{DQ}$

$V_{GSQ}$

$I_{DSS}$


$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$I_D = \frac{V_s}{R_s} = \frac{1.7}{510} = \boxed{3.33 \text{ mA}} = I_s \quad \checkmark$$

$$V_{GS} = V_G - V_s \Rightarrow V_{GS} = -V_s \Rightarrow V_{GS} = \boxed{-1.7 \text{ V}} \quad \checkmark$$

$$I_{DSS} = \frac{I_D}{\left(1 - \frac{V_{GS}}{V_p}\right)^2} = \frac{3.33 \text{ mA}}{\left(1 - \frac{-1.7}{-4}\right)^2} = \boxed{10.07 \text{ mA}}$$

6

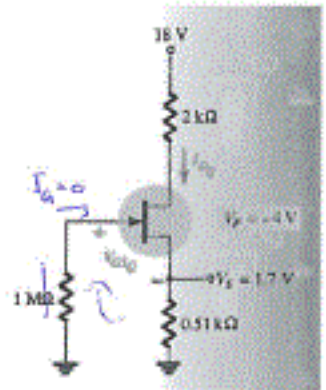

b) For the fixed biased configuration Determine


$V_{GSQ}$

$I_{DQ}$

$V_{DS}$

$$V_{GS} = -V_{GG} = \boxed{-2 \text{ V}} \quad \checkmark$$
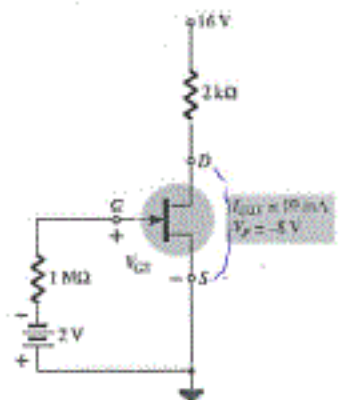
$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 = (10 \text{ mA}) \left(1 - \frac{-2}{-3}\right)^2 = \boxed{5.625 \text{ mA}}$$




$$V_{DS} = V_{DD} - I_D R_D \quad \text{no resistor in source terminal}$$

$$V_{DS} = 16 - (5.625 \text{ mA}) (2 \text{ k}\Omega) = \boxed{4.75 \text{ V}}$$


**Question 4 (10 points)**

Find and compare the value of Input/Output Impedance and voltage gain of the given Common base and Common Emitter configuration

**Solution**

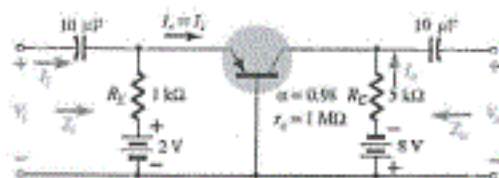

if we draw small signal

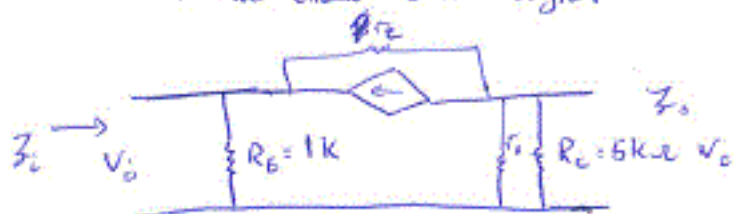

$$Z_i = R_E \parallel r_e$$

$$I_E = \frac{2 \cdot 10^{-3}}{1k} = 2 \text{ mA}$$

$$r_e = \frac{26m}{2m} = 13 \Omega$$



$$A_v = -\alpha = -0.98$$

$$Z_o = R_C = 5k \Omega$$

because  $r_o \gg R_C$

$$Z_i = 12.83 \Omega$$
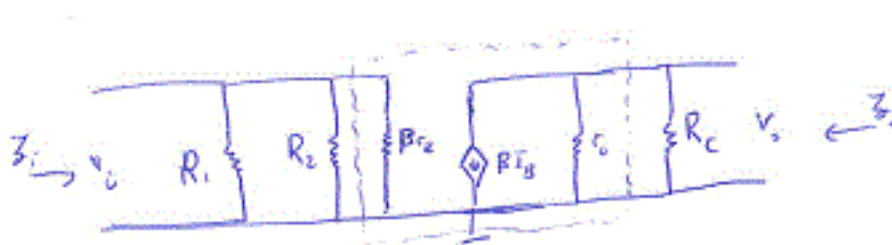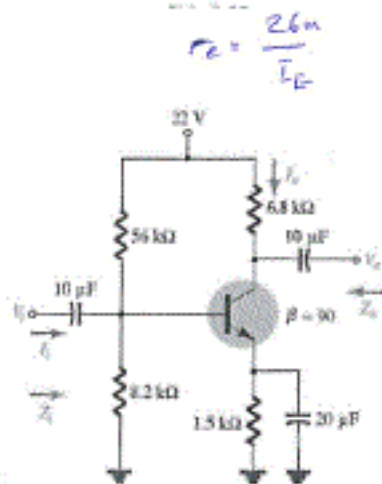
$$A_v = \frac{V_o}{V_i} = \frac{R_C}{r_e} = \frac{5k}{13} = 384.61 \text{ V}$$



$$Z_i = R_1 \parallel R_2 \parallel \beta r_e$$

$$V_{BE} = V_B - V_E$$

$$0.7 = 2.81 - V_E$$

$$V_E = 2.81 - 0.7 = 2.11 \text{ V}$$

$$I_E = \frac{2.11}{1.5k} = 1.407 \text{ mA}$$

$$r_e = \frac{26m}{1.407m} = 18.48 \Omega$$

$$r_e = \frac{26m}{I_E} = \frac{26m}{1.407m}$$

$$V_B = \frac{22 \times 2.2k}{2.2k + 56k} = 2.81 \text{ V}$$

$$Z_i = \frac{7152.65 \times 18.48 \times 40}{7152.65 + 18.48 \times 40} = 134942 \Omega$$


$$Z_o = R_C = 6.8k \Omega$$

$$A_v = \frac{V_o}{V_i} = \frac{-R_C}{r_e} = -367.96 \text{ V}$$

**Question 3 (10 points)**

(a) For the given circuit calculate maximum  $V_i$  that will maintain  $V_i$  (Vload) to 8V and not exceed the power rating of diode

**Solution**

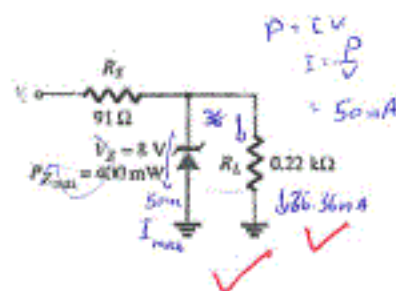

~~8~~  $8 = \frac{V_{i \min} (0.22k)}{(91) + (0.22k)}$

$V_{i \min} = \frac{8(91 + 0.22k)}{0.22k} = \boxed{11.31V}$  this min  $V_i$


$V_{i \max} = V_Z + I R_S$

$= 8 + (50)(91) = \boxed{12.55V}$

$(50 + 36.36)(91) = 15.86$

4

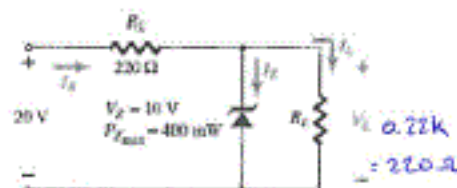b) Determine  $V_L$ ,  $I_{R_L}$ ,  $I_Z$ ,  $I_{R_S}$  for the given Zener diode circuit



$V_L = \frac{20 \times 0.22k}{0.22k + 220} = \boxed{10V}$

$I_{R_L} = \frac{10}{0.22k} = \boxed{45.45mA}$

$I_Z = \frac{P}{V} = \frac{400m}{10} = \boxed{40mA}$   $45.45 - 40 = \boxed{5.45mA}$

~~Handwritten scribbles~~

$I_R = I_Z + I_{R_L} = 45.45m + 5.45m = \boxed{50.9mA}$

**Question 2 (10 points)**




a) For the Diode rectifier circuit draw the output wave form with correct voltage levels.

What is average DC value at the output? (5)



$$V_{dc} = 0.636 V_m$$

$$= 0.636(50)$$

$$= 31.8 V$$

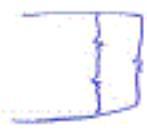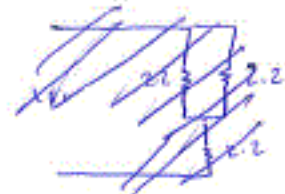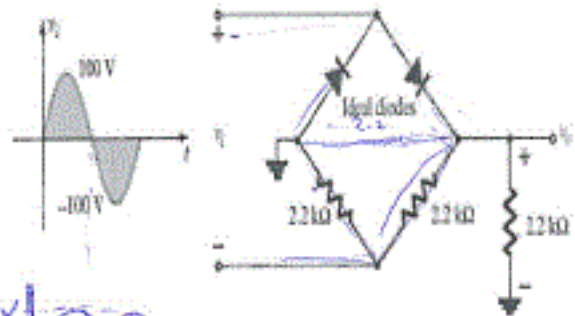

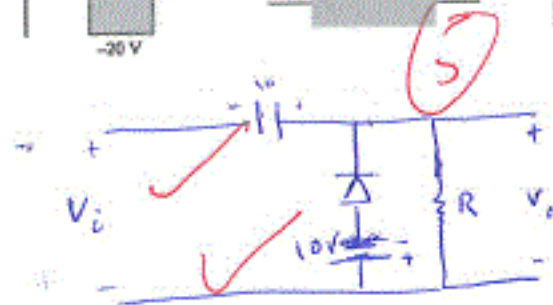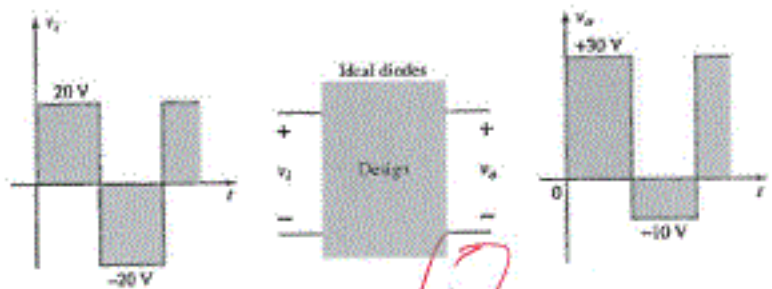b) Design the diode circuit according to given specs (5)



Question 1 (8 points)

- (a) Explain semiconductor material. How n-type and P-type material are formed. (4)  
 (b) Explain semiconductor diode. Show characteristic curve for semiconductor diode. (4)  
 (c) Explain how LED works. (2)

Solution


a) Semiconductor material is between conductor and insulator material like silicon. ✓

We can form n-type material by add Pentavalent elements so that the majority is electrons <sub>carrier</sub> ✓

The P-type material can be formed by add trivalent ~~type~~ elements and the majority carrier is holes. ✓  
 (4)

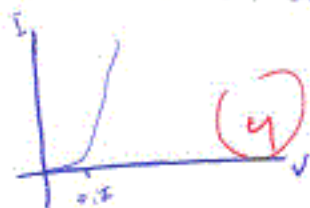b) Semiconductor diode is formed by N-type and P-type materials, and called NP junction

it has a polarity so if you want to connect it you have to connect the  $\ominus$  side of battery with N and  $\oplus$  with P other wise the depletion region will get bigger until it reach the breakdown voltage and then burn.



for silicon diode it will start conduct in 0.7V ✓

c) LED is light emitting diode and formed by Gallium arsenide when you connect it to voltage source the photons start moving. ✓  
 (1)



EE 212 - ELECTRONICS II

Fall Semester 2017-2018

Final Exam

Exam Date: December 31, 2017; Exam Duration: 120 minutes

Student's Full Name: \_\_\_\_\_

Student ID #: \_\_\_\_\_ Section #: 1050 Signature: \_\_\_\_\_

Instructions:

- Write your student ID number on the top of each page
- Write the solution in the space provided under each question
- Show all the details of your analysis and calculations

*Good work  
keep it  
up.*

Question No.	Points Assigned	Points Awarded
1. [CO_1, PI_1_45, SO_1]	10	9
2. [CO_3, PI_5_51, SO_5]	10	10
3. [CO_4, PI_1_74, SO_1]	10	9
4. [CO_6, PI_1_72, SO_1]	10	10
5. [CO_8, PI_5_52, SO_5]	10	10
6. [CO_9, PI_5_54, SO_5]	10	10
Total	60	59

Instructor's Full Name	Dr. Abdul Waheed Malik
Signature	<i>Abdul Waheed Malik</i>